

## Experiment Number- 6

**Title:** IMPEDANCE MEASUREMENT

**Aim:** i) To measure the resistance and inductance of a choke coil.  
ii) To measure the resistance and capacitance of a non ideal capacitor.

**Apparatus required:**



Sl.	Name of Equipments	Specification	Quantity
1	Regulated DC power supply		
2	Variac		
3	Voltmeter (MI)		
4	Voltmeter (MC)		
5	Ammeter (MI)		
6	Ammeter (MC)		
7	Wattmeter		
8	Choke coil		
9	Capacitor		
10	Connecting wire		

**Theory**

**Procedure:**

- a) Measurement of resistance and inductance of a choke coil
  - i) Connect the circuit as in figure 1
  - ii) Vary the value of supply voltage (DC) from minimum to maximum
  - iii) Note the value of voltage and current in table 1
  - iv) Plot a graph between voltage and current
  - v) Calculate the value of resistance from the slope of the graph
  - vi) Connect the circuit as in figure 2
  - vii) Repeat step (ii) , (iii), (iv) with AC source
  - viii) Calculate the value of impedance from the slope of the graph
  - ix) Calculate the inductance of the coil.
- b) Measurement of resistance and capacitance of a non ideal capacitor
  - i) Connect the circuit as in figure 1
  - ii) Vary the value of supply voltage from minimum to maximum

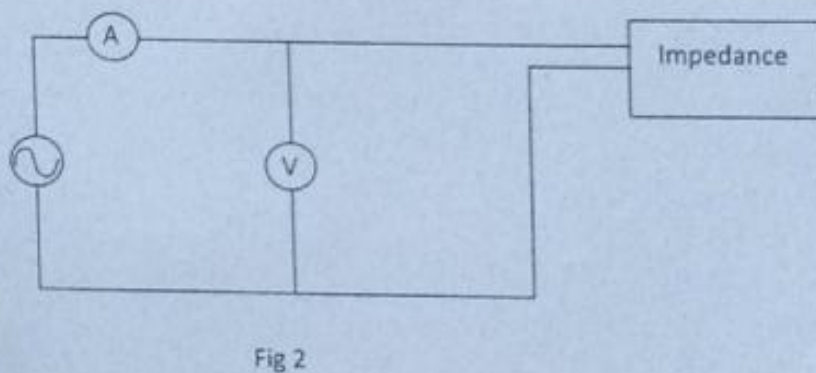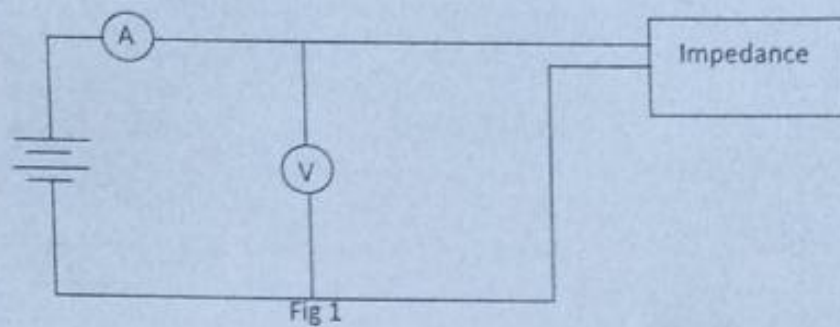- iii) Note the value of voltage and current in table 3
- iv) Plot a graph between voltage and current
- v) Calculate the value of resistance from the slope of the graph
- vi) Connect the circuit as in figure 2
- vii) Repeat step (ii), (iii), (iv) with AC source
- viii) Calculate the value of impedance from the slope of the graph
- ix) Calculate the capacitance.



### Observation

Table1: Table for finding resistance of the coil

Sl.No	Voltage (V)	Current (i)



Table2: Table for finding impedance of the coil

Sl.No	Voltage (V)	Current (i)

Table 3: Table for finding resistance of non ideal capacitor

Sl.No	Voltage (V)	Current (i)

Table 4: Table for finding impedance of non ideal capacitor

Sl.No	Voltage (V)	Current (i)

**Calculation:-**

**Precaution:-**

**Discussion:-**

- e) Consider a coupled inductor (say a transformer). How will you experimentally determine the value of  $L_1$ ,  $L_2$  and  $M$ .