

Experiment Number- 5

Title: POWER AND ENERGY MEASUREMENT.

Aim: i) To measure the Power, Energy and Power factor in a single phase AC circuit using analog meter

Apparatus required:

Sl.	Name of Equipments	Specification	Quantity
1	Variac		
2	Voltmeter (MI)		
3	Ammeter (MI)		
4	Wattmeter		
6	Choke coil		
7	Resistive load		
8	Connecting wire		

Theory

Procedure:

- i) Connect the circuit as shown in figure 1
- ii) Connect a resistive load
- iii) Note down the readings of ammeter, voltmeter, wattmeter and energy-meter
- iv) Calculate the phase difference
- v) Repeat step (ii), (iii) and (iv) with RL load.
- vi) Connect the circuit as shown in figure 2
- vii) Measure the voltage and current across the load using a CRO.
- viii) Find the RMS values of voltage and current and note the reading in table 2
- ix) Find the phase difference from time difference between the waveform of current and voltage as observed in the CRO.
- x) Calculate the power as $VI\cos\theta$.

Observation

Table1: Table showing the power energy and frequency measurement in a AC circuit from analog meter

Sl. No	Voltage (V)	Current (A)	Power(W)	Frequency (Hz)	Power factor (W/VI)	Energy consumed in 5 min	Type of load

Table2 : Table showing the power energy and frequency measurement in a AC circuit from CRO

Sl. No	Voltage (V)	Current (A)	Power(W)	Frequency (Hz)	Power factor	Type of load

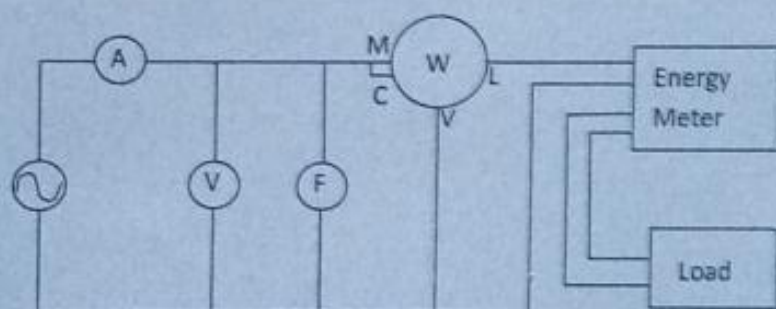


Fig 1



Fig 2

Calculation:-

Precaution:-

Discussion:-

Explain how power can be measured in a three phase circuit if

- a) Both load and source are balanced.
- b) Source is balanced but load is not balanced.
- c) Load is balanced but source is not balanced.
- d) Both source and load are unbalanced.