

## Experiment No.- 9

**Title:** AC Bridge.

**Aim:**

- (i) To measure the resistance and inductance using Anderson's bridge.

**Apparatus required:**

Sl. No.	Name of component/apparatus	Specification	Quantity
1	Anderson's bridge Trainer		
2	Wien bridge Trainer		
3	Capacitor		
4	Inductor		
5	Resistor		
6	Variable resistance		
7	Multimeter		

**Theory:**

**Procedure:**

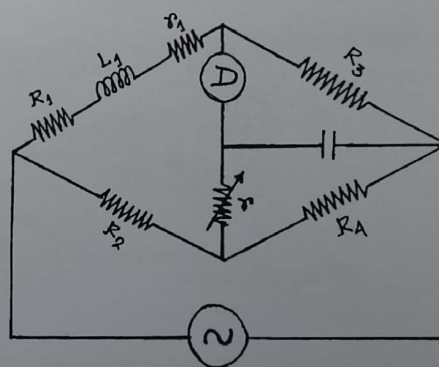


Fig: Anderson's Bridge

### 1. Anderson's bridge:

- Connect the trainer circuit to form an Anderson's bridge.
- Adjust the value of resistance to get a null.
- Calculate the value of the resistance and inductance.

**Observation:**

**(a) Anderson's bridge:**

Sl. No.	Value of r	Value of r	$L = C \frac{R_3}{R_4} \left( r(R_2 + R_4) + R_2 R_4 \right)$

**Result:**

**Precautions:**

**Conclusion:**

Project: To design and fabricate a suitable AC bridge and measure relevant parameters

### Experiment No: 10

**Title:** DC Bridge.

**Aim:**

1) DC POTENTIOMETER & CALIBRATION OF AMMETER.

**Apparatus required:**

Sl. No	Name of equipments	Specification	Quantity

DC potentiometer:

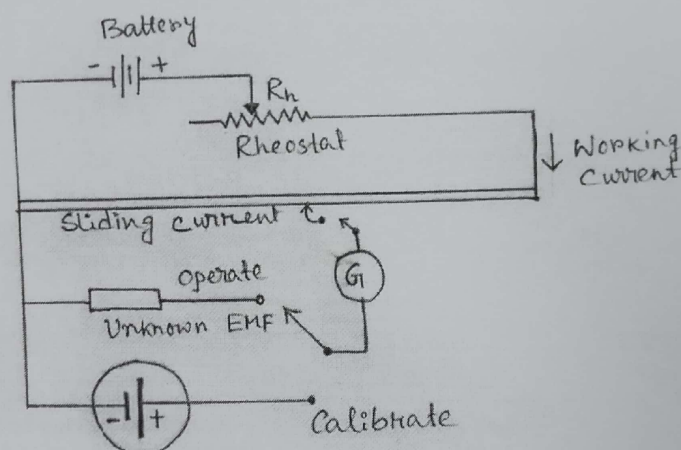


Fig: DC potentiometer circuit

### PROCEDURE:

DC potentiometer:

- (1) Connect emf (standard) to dc potentiometer.
- (2) Adjust the dial to the known value of emf.
- (3) Vary  $P_1$  and  $P_2$  until Galvanometer shows null.
- (4) Compare the result with multimeter.

Observation table:

RANGE SELECT	DIAL READING	LEAST COUNT(mV)	VOLTAGE MEASURED BY POTENTIOMETER

RESULT:

PRECAUTIONS:

CONCLUSION:

### Experiment No: 11

**Title:** Measurement of earth resistance and insulation resistance.

**Aim:**

- 1) To measure earth resistance.
- 2) To measure the insulation resistance of different electrical machines.

**Apparatus required:**

SL. No.	Name of the Equipment	Specification	Quantity
1	Earth tester		
2	Auxiliary electrodes		
3	Connecting wires		
4	Megger		

**Theory:**

**Procedure:**

**A) Measurement of earth resistance:**

- 1) Connect "E" terminal of earth tester to earth electrode.
- 2) Insert auxiliary electrode at specified distance.
- 3) Connect "C" and "P" terminal to auxiliary electrode.
- 4) Measure earth resistance.
- 5) Vary distance and repeat measurement.
- 6) Plot a graph between earth resistance and distance.

**B) Measurement of Insulation resistance:**

- 1) Disconnect the machine and open all connections
- 2) Measure the insulation resistance between field and earth, armature and earth and field and armature of machine.

**Observation:**

**To measure earth resistance:**

SL. No.	Distance (feet)	Resistance (Ohms)

**To measure Insulation resistance:**

Armature insulator resistance =  
Field insulator resistance =  
Armature-Field resistance =

**Results:**

**Precaution:**

**Conclusion:**



### EXPERIMENT: 7

**Title:** Phase Difference and frequency measurement.



**Objective:-**

- To measure Phase Difference between two wave form using DSO.
- To measure unknown frequency from lissajous figure using DSO.

**Apparatus Required:**

	Name	Specification	Quantity

**Circuit Diagram:**

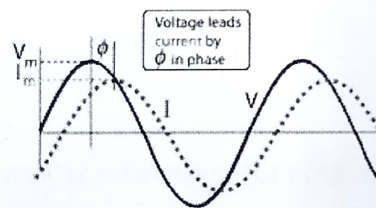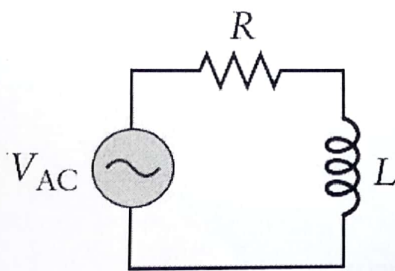

**Theory:** Elliptical pattern for different combinations of R & L values:



The Phase angle is calculated as

$$\sin \theta = A/B$$

$$\text{Or, } \theta = \sin^{-1} (A/B)$$

Where, A = distance between the points where ellipse crosses the Y axis and the origin

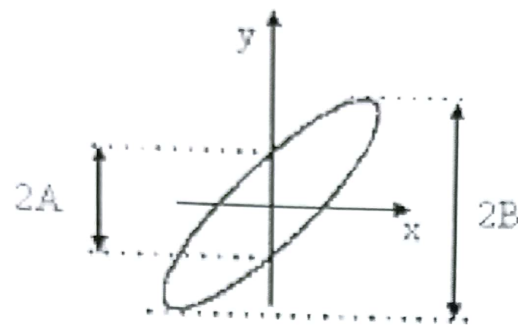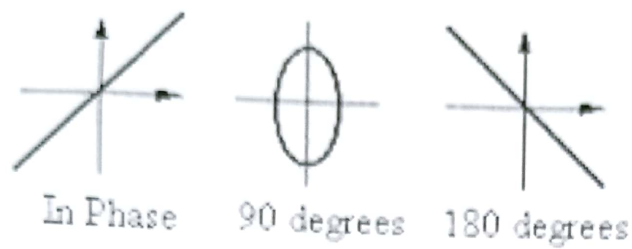B = distance between the points the origin and Y axis of the maxima of the ellipse.



General Phase Difference

$$\sin \Theta = \frac{A}{B}$$

### Procedure:

#### a) PHASE DIFFERENCE MEASUREMENT:

To measure the Phase difference of two Sine Waves, their frequency must be equal.

- Connect the circuit as per the diagram.
- Connect and apply a 2V peak-peak 50Hz sine wave from the function generator to the CH1 of the CRO.
- Connect the output of phase shift network to the CH2 of the CRO.
- Observe the waveform in Y-T mode and Lissajous figure in X-Y mode for different combination of R & L values.

#### b) FREQUENCY MEASUREMENT:

- Connect the two power supply with different frequency with the help of two Function Generators.
- Observe the no of Peaks in X axis and Y axis in X-Y mode.
- Take the ratio of no of peaks in X-axis to that of Y-axis of Lissajous pattern and compare with the ratio of both input frequency.



**Observation:**

**Table-1 : For Measurement of Phase Difference**

Sl No	Resistance	No. of Div. for $180^\circ$	Least count	D (Div.)	d (Div.)	d/D	Phase Difference	
							Y-T mode Degree	X-Y mode Degree

**Table-2 : For Frequency Phase Difference**

Sl No	Frequency (Hz)		No. of turns(peaks)		Peaks Ratio
	F1(FY)	F2 (FX)	Along Y-axis	Along X-axis	$Y/X = F_Y/F_X$

**Calculations:-**

**Result & Conclusion:-**

**Precaution:-**

**Discussion:-**