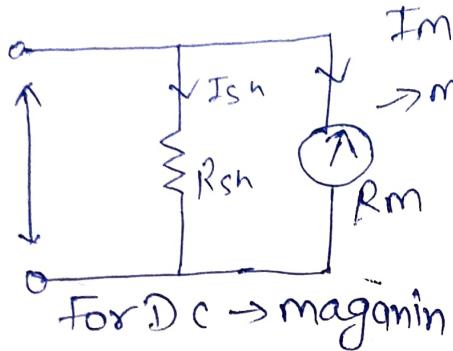


16/08/2022

Measurement and Measuring Instrument

Ammeter shunt



$m = \text{multiplying power of shunt}$

$$I = I_{sh} + I_m$$


$$I_{sh} = -I_m + I$$

$$I_{sh} = I - I_m$$

$$I_{sh} R_{sh} = I_m R_m$$

$$R_{sh} = \frac{I_m R_m}{I - I_m} = \frac{R_m}{\frac{I - I_m}{I_m}} = \frac{R_m}{m - 1}$$

Arrangement for temp. effect Correction

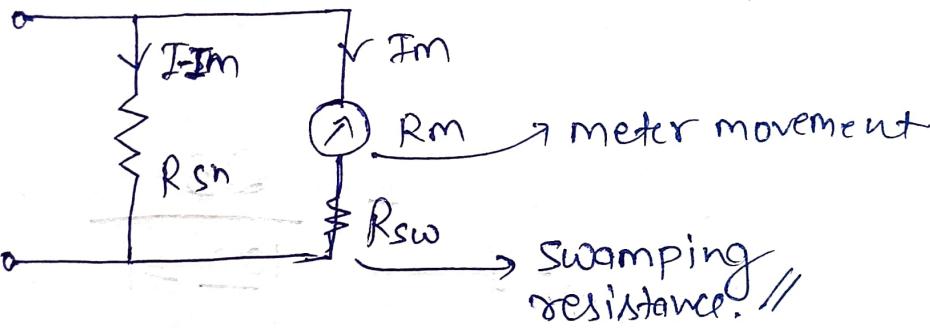

For DC Suitable material - manganin

for AC → Constantan.

Swamping resistor is used for temp. Compensation

- Q) A moving coil instrument whose resistance is 25Ω gives a full scale deflection with a current of $1mA$. This instrument is to be used with a manganin shunt to extend its range to $100mA$.

Calculate the error caused by the 10°C rise in temp.

when -

- (1) copper moving coil is connected directly across a manganese shunt.
- (2) A 75Ω manganese resistance is used in series with instrument moving coil.

The temp. coefficient of copper is $0.004/\text{ }^{\circ}\text{C}$ and for manganese $0.00015/\text{ }^{\circ}\text{C}$.

$$R_{sh} = \frac{R_m}{I/I_m - 1} = \frac{25}{\frac{100}{1} - 1}$$

$$R_{sh} \Rightarrow \frac{25}{99} = 0.2525\Omega$$

for 10°C ↑

$$R_t = R_0(1 + \alpha t) \text{ for } 10^{\circ}\text{C}$$




$$R_m' = 25(1 + 0.004 \times 10) = 26\Omega$$

$$R_{sh}' = 0.2525(1 + 0.00015 \times 10) \\ = 0.2520\Omega$$

$$I_m' = \frac{100 \times 0.2520}{0.2520 + 26} = 0.96$$

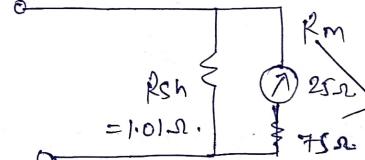
$$\% \text{ error} = \frac{0.96 - 1}{1} \times 100 \\ = -4\%$$



$$R_{sh} = \frac{R_{mt}}{m-1}$$

$$= \frac{R_{mt}}{\frac{100}{100-1}} = \frac{100}{100/99} = 1.01\Omega$$

for 10°C rise.

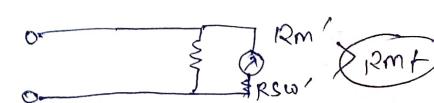

$$\frac{R_{mt}'}{R_{sh}'} =$$


$$\frac{R_{mt}'}{R_{sh}''} = \frac{25(1+0.001 \times 10) + 75(1+0.00015 \times 10)}{1.01(1+0.0015 \times 10)}$$

$$\frac{R_{mt}'}{R_{sh}''} = \frac{101.102 \Omega}{1.011 \cdot 2}$$


$$I_m'' = 100 \times \frac{1.01}{1.011 - 101.102} = 0.99 A.$$

$$\Rightarrow \frac{0.99 - 1}{1} \times 100 = -1\%$$

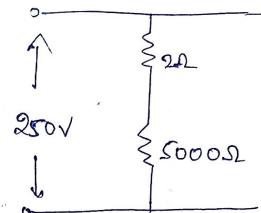Q) A moving coil instrument has a resistance of 2Ω and it reads upto 250 volt, When a resistance of 5000Ω is connected in series with it, find the current range of instrument when it is used as an ammeter with the coil connected across the shunt resistance of $2m\Omega$.


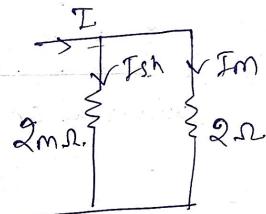
$$I_m = \frac{250}{2 + 5000} = 0.0499 A$$



$$I_{sh} R_{sh} = I_m R_m$$

$$I_{sh} = \frac{R_m I_m}{R_{sh}}$$


$$I_{sh} = 49.9 A$$

$$I = I_m + I_{sh}$$

$$= 0.0499 + 49.9 A = 49.949 A$$

Q) Design a multi-range dc ammeter using a basic movement with an internal resistance of 50Ω and a full scale deflection current $I_m = 1mA$. The ranges required are $0-1A$, $0-50A$, $0-10A$.


Multi-range ammeter

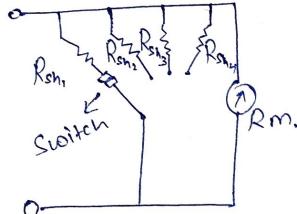

$$(I_1 - I_m) R_{sh1} = I_m R_m$$

$$R_{sh1} = \frac{I_m R_m}{I_1 - I_m}$$
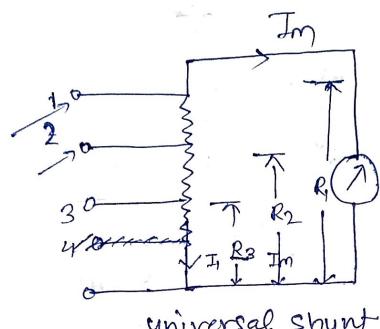
$$= \frac{R_m}{\frac{I_1}{I_m} - 1} = \frac{R_m}{M_1 - 1}$$



for R_1

$$(I_1 - I_m) R_1 = R_m I_m$$

$$R_1 = \frac{R_m I_m}{I_1 - I_m}$$

$$R_1 = \frac{R_m}{\frac{I_1}{I_m} - 1} = \frac{R_m}{M_1 - 1}$$

for R_2

$$(I_2 - I_m) R_2 = (R_1 - R_2 + R_m) I_m$$

$$R_2 R_2 - I_m R_2 = I_m R_1 - R_2 I_m + I_m R_m$$

$$R_2 = \frac{I_m (R_1 + R_m)}{I_2}$$

$$R_2 = \frac{R_1 + R_m}{\frac{I_m}{M_2}} = \frac{R_1 + R_m}{M_2}$$

for R_3

$$(I_3 - I_m) R_3 = (R_1 - R_3 + R_m) I_m$$

$$I_3 R_3 - I_m R_3 = I_m R_1 - R_3 I_m + I_m R_m$$

$$I_3 R_3 = I_m (R_1 + R_m)$$

$$R_3 = \frac{R_1 + R_m}{\frac{I_3}{I_m}} = \frac{R_1 + R_m}{M_3}$$

Soln 1)

$$R_1 = \frac{R_m}{M_1 - 1} \Rightarrow \frac{50}{\frac{1}{10^{-3}} - 1} = \frac{50}{999} = 0.05$$

$$R_2 = \frac{R_1 + R_m}{M_2} \Rightarrow \frac{50 + 50}{10} \Rightarrow 0.01 \Omega$$


$$R_3 = \frac{R_1 + R_m}{M_3} \Rightarrow \frac{\frac{50}{10^{-3}} + 50}{1000} \Rightarrow 0.005$$

$$\therefore \gamma_1 = R_1 - R_2 = 0.04\Omega$$

$$\gamma_2 = R_2 - R_3 = 0.005\Omega$$

$$\gamma_3 = R_3 = 0.005\Omega$$

Voltmeter Multiplier

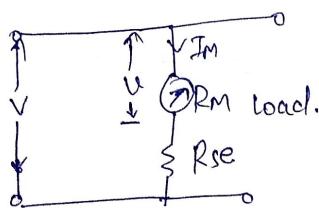

$$V = I_m R_m, I_m = \frac{V}{R_m}$$

$$V = I_m (R_m + R_{se})$$

$$R_{se} + R_m = \frac{V}{I_m}$$

$$R_{se} = \frac{V}{I_m} - R_m \\ = \frac{V}{M R_m} - R_m$$

$$= M R_m - R_m \\ \Rightarrow R_m (M-1)$$

$$R_{se} = R_m (M-1)$$

Q) A moving coil instrument has a resistance of 10Ω and gives full scale deflection when carrying a current of $50mA$. Show how it can be adopted to measure Voltage upto 750 volt and Current upto 1000A.

$$R_{sh} = \frac{R_m}{M-1} = \frac{R_m}{\frac{V}{I_m}} = \frac{10}{\frac{750}{50 \times 10^{-3}}} = \frac{10}{15000} = 0.0005 \Omega$$


$$R_{se} = R_m (M-1)$$

$$R_{se} \Rightarrow \frac{V}{I_m} - R_m$$



$$\Rightarrow \frac{750}{50} = 15 \\ \Rightarrow 14990$$

10/07/2022

MULTIRANGE DC VOLTMETER

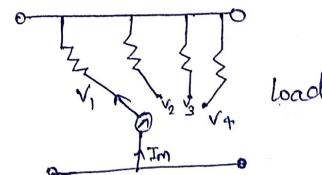

Individual Multipliers

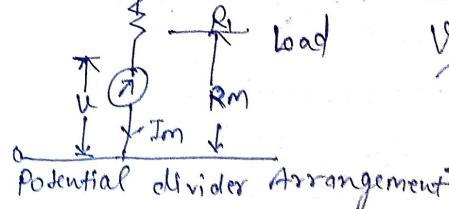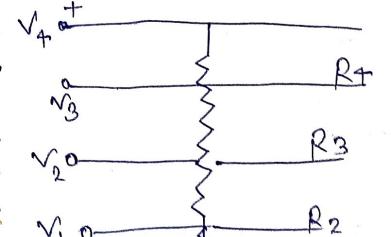

$$V = I_m R_m \\ I_m = \frac{V}{R_m}$$

$$R_{s1} = \frac{V_1}{I_m} - R_m$$

$$= \frac{V_1}{M_1 R_m} - R_m$$

$$= M_1 R_m - R_m$$

$$R_{s1} = R_m (M_1 - 1)$$

$$\frac{V_1}{V_o} = M_1,$$

$$R_{s2} = R_m (M_2 - 1)$$

$$R_{s3} = R_m (M_3 - 1)$$

for R₁

$$V = Im R_m \rightarrow Im = \frac{V}{R_m} \Rightarrow \frac{V}{Im} = M_1$$

$$V_1 = Im (R_1 + R_m)$$

$$R_1 = \frac{V_1}{Im} - R_m$$

$$= \frac{V_1}{\cancel{Im}} - R_m$$

$$= M_1 R_m - R_m$$

$$\boxed{R_1 = R_m (M_1 - 1)}$$

for R₂

$$V_2 = Im (R_2 + R_1 + R_m)$$

$$R_2 = \frac{V_2}{Im} - R_1 - R_m$$

$$= \frac{V_2}{\cancel{Im}} - R_m (M_1 - 1) - R_m$$

$$= M_2 R_m - R_m M_1 + R_m - R_m$$

$$\boxed{R_2 \Rightarrow R_m (M_2 - M_1)}$$

for R₃

$$V_3 = Im (R_m + R_1 + R_2 + R_3)$$

$$R_3 = \frac{V_3}{Im} - R_m - R_1 - R_2$$

$$R_3 = M_3 R_m - R_m - R_m M_1 + R_m \\ - R_m M_2 + M_1 R_m$$

$$R_3 = R_m (M_3 - M_2)$$

for R₄

$$V_4 = Im (R_m + R_1 + R_2 + R_3 + R_4)$$

$$R_4 = \frac{V_4}{Im} - R_m - R_1 - R_2 - R_3$$

$$= M_4 R_m - R_m - R_m (M_1 - 1) - \\ R_m (M_3 - M_1)$$

$$R_4 = R_m (M_4 - M_3)$$

- Q) A basic meter movement, with an internal resistance $R_m = 100\Omega$ and full scale current $Im = 1mA$ is to be converted into a multirange dc voltmeter with ranges $0-10V$, $0-150V$, $0-250V$, $0-500V$. find the values of various resistances, using potential divider arrays.

0-10, 0-50, 0-250, 0-500

$$R_s = R_m(M_i - 1)$$

$$R_s = 100 \left(\frac{V_s}{V} - 1 \right)$$

$$R_s = \frac{10}{10^{-3}} f. 100$$

$$R_s = 100000 - 100$$

$$= 99,900$$

$$R_2 = \frac{50}{10^3} - 99900 - 100$$

$$\Rightarrow 400,000$$

$$R_3 \Rightarrow 250 \times 10^3 - 400000 -$$

$$99900 - 100$$

$$R_3 = 200 \text{ k}\Omega$$

$$R_4 \Rightarrow 500 \times 10^3 - 2000,000 - 400000$$

$$- 99900 - 100$$

$$\Rightarrow 250 \text{ k}\Omega$$

- A moving coil ammeter is a fixed shunt of 0.02Ω with a coil resistance $R = 100 \Omega$ and a potential difference of 500 mV across it, full scale deflection is obtained -
- To what shunted current does this correspond?
 - Calculate the value of R to give full scale deflection when shunted current I_{sh}
a) 10 A, b) 75 A
 - With what value of R is 10% deflection is obtained with $I_{sh} = 100 \text{ A}$


Soln

$$500 \times 10^{-3} \approx I_m (1000 + 0.02)$$

$$g) R = 100 \Omega$$

$$V = 0.05 \text{ V}$$

$$R_{sh} = 0.02 \Omega$$

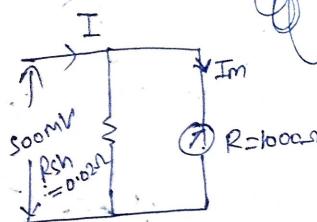

$$I_{sh} = \frac{V}{R_{sh}} = \frac{0.05 \times 10}{0.02} \Rightarrow 25 \text{ A} = I_{sh}$$

$$(I_m = \frac{0.5}{10^3} \text{ A})$$

ii)

$$R = \frac{0.2}{I_m \times 10^{-3}} = 400 \Omega$$

$$V_{sh} = I_m \times R_{sh} = 0.05 \times 10^{-3} \times 250 = 0.00125 \text{ V}$$

$$R = \frac{1.5}{0.05 \times 10^{-3}} = 3000 \Omega$$

$$\begin{aligned} & V_{sh} = I_m \cdot R_{sh} \\ & = 0.05 \times 10^{-3} \times 250 \\ & = 0.00125 \text{ V} \\ & \downarrow \\ & R = \frac{1.5}{0.05 \times 10^{-3}} = 3000 \Omega \end{aligned}$$

$$\text{Vol. across shunt} = 0.02 \times 250$$




$\Rightarrow S = 5V$

$$R = \frac{S}{0.5 \times 10^{-3}} = 10 \Omega = 10 \text{ k}\Omega$$


$x \rightarrow \frac{100}{70} \%$
 $x \rightarrow 28.57\%$

Moving Iron Instruments

23/08/2022

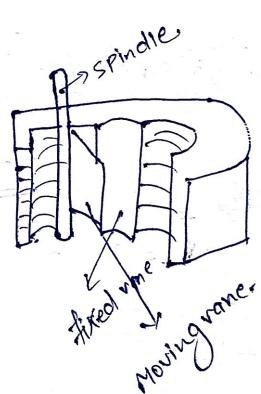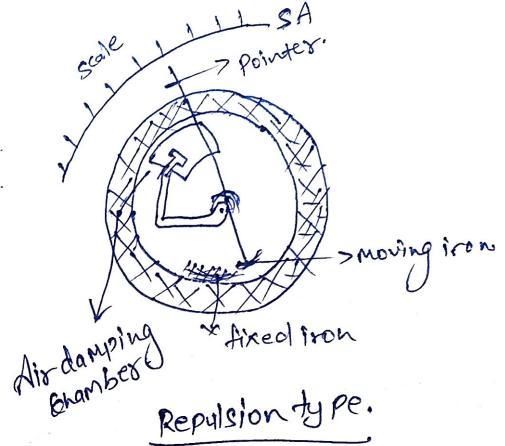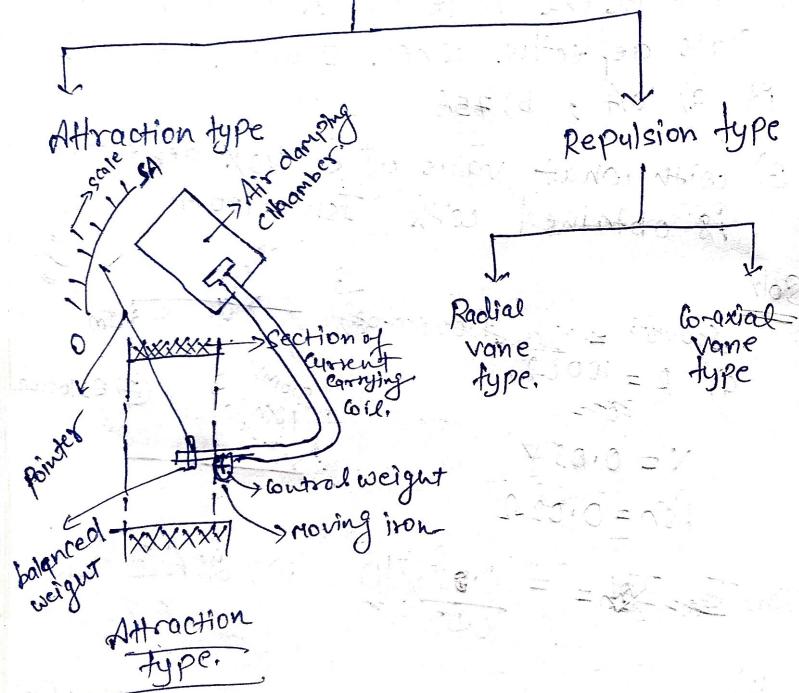

Radial vane type.

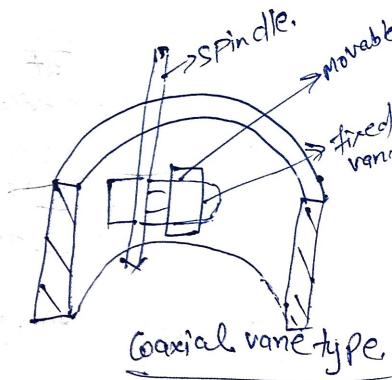

MOVING IRON INSTRUMENT

24/08/2022

General torque equation -

$T_d \rightarrow$ deflecting torque
 $\theta \rightarrow$ deflection.

\therefore Mechanical work done = $T_d d\theta$.

$$\because I \rightarrow dI \quad c = \frac{d}{dt}(LI)$$

$$L \rightarrow dL$$

$$\Theta \rightarrow d\theta$$

$$= \frac{Ldi}{dt} + Id\frac{L}{dt} \rightarrow (i)$$

\therefore Electrical energy supplied,

$$= cidi$$

$$\Rightarrow LI di + I^2 dL$$

$$\Rightarrow LI di + I^2 dL \rightarrow (ii)$$

Change in stored energy

$$= \frac{1}{2}(I+di)^2(L+dL) - \frac{1}{2}LI^2$$

$$\Rightarrow \frac{1}{2}(I^2 + (di)^2 + 2Idi)(L+dL) - \frac{1}{2}LI^2$$

$$\Rightarrow \frac{1}{2}[LI^2 + (di)^2 + 2LI di + I^2 dL + dL(di)^2 + 2Idi dL] - \frac{1}{2}LI^2$$

$$\Rightarrow \frac{(di)^2}{2} + \cancel{\frac{2LIdi}{2}} + \cancel{\frac{2Idi dL}{2}} + \frac{I^2 dL}{2} + \frac{dL(di)^2}{2}$$

$\left. \begin{array}{l} \text{neglect } 2nd \\ \text{and higher order} \\ \text{term} \end{array} \right\}$

$$\Rightarrow LI di + \frac{1}{2}I^2 dL$$

$$\therefore LI di + \frac{1}{2}I^2 dL \rightarrow (iii)$$

From principle of conservation of energy

electrical energy supplied = change in stored energy + Mechanical work done.

$$LI di + I^2 dL = LI di + \frac{1}{2}I^2 dL + T_d \cdot d\theta.$$

$$I^2 dL = \frac{1}{2}I^2 dL + T_d \cdot d\theta.$$

$$\frac{1}{2}I^2 dL = T_d \cdot d\theta.$$

$$\boxed{\frac{1}{2}I^2 dL = T_d \cdot d\theta}$$

At steady state position,

$$T_d = T_c \quad \text{and} \quad T_c = K\theta.$$

$$T_d = T_c$$

$$K\theta = \frac{1}{2}I^2 \frac{dL}{d\theta}$$

$$\boxed{\theta = \frac{1}{2} \frac{I^2 dL}{K d\theta}}$$


SCALE OF MOVING IRON INSTRUMENT -

For linear scale.

$$I \propto \theta$$

$$I = C\theta$$
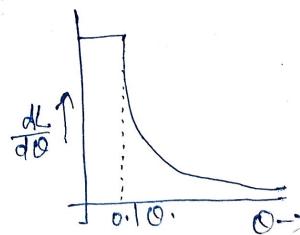
$$\theta = \frac{1}{2} \frac{I^2}{K} \frac{dL}{d\theta}$$




$$\frac{dL}{d\theta} = \frac{2K\theta}{I^2} = \frac{2K\theta}{C^2\theta^2} = \frac{2K}{C^2\theta}$$

$$\frac{dL}{d\theta} = \left(\frac{2K}{C^2}\right)$$

↓
constant

SHUNT IN MOVING IRON INSTRUMENTS

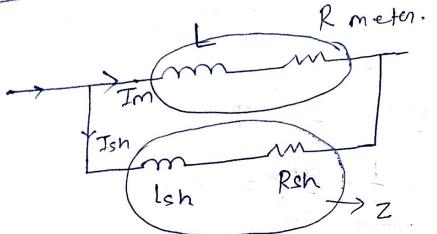

$$Z_1 = \sqrt{R^2 + \omega^2 L^2}$$

$$Z_2 = \sqrt{R_{sh}^2 + \omega^2 L_{sh}^2}$$

$$I_m Z_1 = I_{sh} Z_2$$

$$I_m \times \sqrt{R^2 + \omega^2 L^2} = I_{sh} \times \sqrt{R_{sh}^2 + \omega^2 L_{sh}^2}$$

$$\frac{I_{sh}}{I_m} = \frac{\sqrt{R^2 + \omega^2 L^2}}{\sqrt{R_{sh}^2 + \omega^2 L_{sh}^2}} = \frac{R \sqrt{1 + \left(\frac{\omega L}{R}\right)^2}}{R_{sh} \sqrt{\left(1 + \frac{\omega L_{sh}}{R_{sh}}\right)^2}}$$

For frequency independent -

$$\frac{L}{R} = \frac{L_{sh}}{R_{sh}}, \text{ then } \frac{I_{sh}}{I_m} = \frac{R}{R_{sh}}$$

Q) The inductance of a moving iron ammeter is given by, the following equation-

$$L = (20 + 10\theta + 2\theta^2) \mu H$$

θ → is the deflection in radians, $K = 24 \times 10^{-6} \text{ NM/A}$

Calculate the value of deflection of A current of 5A

$$\begin{aligned} L &= 10 - 5\theta + 2\theta^2 \\ \frac{dL}{d\theta} &\Rightarrow 0 + 5 + 4\theta \\ \theta &= \frac{1}{2} \frac{I^2}{K} \frac{dL}{d\theta}. \end{aligned}$$

$$L \Rightarrow -20^2 + 10\theta + 20$$

$$\frac{dL}{d\theta} \Rightarrow -4\theta + 10$$

$$\theta = \frac{1}{2} \frac{(25)}{24 \times 10^{-6}} \times (40 + 10) \times 10^{-6} \quad \frac{\pi}{6} = \frac{1}{2} (100) \cdot \frac{5}{6}$$

$$\theta = \frac{2.5 \times 10^6}{40} (10 - 40)$$

$$\theta = \frac{2.5 \times 10^7}{40} - \frac{2.5 \times 10^6 \times 40}{40}$$

$$\frac{\pi}{6} = \frac{50}{K} \cdot \frac{5}{6}$$

$$K \Rightarrow \frac{50 \times 6}{\pi} \cdot \frac{5}{6}$$

$$K \Rightarrow \frac{300}{\pi} (1.26)$$

$$* \Rightarrow 120.9$$

$$48.0 \times \theta \Rightarrow \frac{2.5}{40 \times 10^{-6}} (-40 + 10) \times 10^{-6}$$

$$\frac{100}{25} + 40 = 10$$


$$K = \frac{2.5 \times \pi}{2 \times 6} (126)$$

$$\frac{100}{25} = 10 \quad \theta \Rightarrow \frac{250}{170} = 1.689$$

Ams

MULTIPLIERS FOR MOVING IRON INSTRUMENTS

25/08/2022

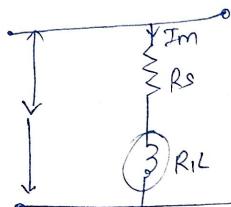

$$V = I_m \sqrt{R^2 + \omega^2 L^2}$$

$$V = I_m \sqrt{(R+R_s)^2 + \omega^2 L^2}$$

$$M = \frac{V}{V_s} = \frac{I_m \sqrt{(R+R_s)^2 + \omega^2 L^2}}{I_m \sqrt{R^2 + \omega^2 L^2}}$$

$$M = \frac{\sqrt{(R+R_s)^2 + \omega^2 L^2}}{\sqrt{R^2 + \omega^2 L^2}}$$

Q1) Calculate the Constant of M to extend the range of (0-5)A moving Iron Ammeter to (0-50)A. The instrument const. are.

$$R = 0.09\Omega$$

$L = 90\mu H$. If the shunt is made non inductive and the combination is correct on DC. Find the full scale error at 50 Hz.

Soln

~~$\frac{I}{I_m} = \frac{R}{R_s}$~~ , $\omega = 10\pi$

$$\frac{L}{R} = \frac{Lsh}{Rsh}, \Rightarrow \frac{90\mu H}{0.09} = \frac{Lsh}{Rsh}$$

$$\frac{Ish}{Im} = \frac{R}{Rsh} \Rightarrow \cancel{\frac{Ish}{Im} = \frac{0.09}{Rsh}} \quad Rsh = 0.09\Omega$$

$$\begin{aligned} & \cancel{0.09} \quad \frac{90\mu H}{0.09} = \frac{Lsh}{0.09} \\ & \cancel{0.09} \times 90 \times 10^{-6} = Lsh \\ & 900 \mu H = Lsh \end{aligned}$$

$$Im = 5A$$

$$I = 50A$$

$$\frac{L}{R} = \frac{Lsh}{Rsh}$$

$$\frac{Ish}{Im} = \frac{R}{Rsh}$$

$$I = Ish + Im$$

$$= \frac{R}{Rsh} \cdot Im + Im$$

$$\frac{I}{Im} = \left(1 + \frac{R}{Rsh}\right) Im$$

$$\frac{I}{Im} = m = 1 + \frac{R}{Rsh}$$

$$Ish = \frac{R}{Rsh} Im$$

$$\therefore Lsh = \frac{L}{R} \times Rsh \\ = 10\mu H$$

$$Rsh = \frac{R}{m-1} = 0.01$$

for DC

$$Im = I \times \frac{Rsh}{R+Rsh}$$

$$\Rightarrow 50 \times \frac{0.01 \times 10^{-6}}{0.01 \times 10^{-6}} = 50$$

$$\frac{Ish}{Im} = \frac{R}{Rsh}$$

2 → ~~3~~ → Network
 3 → ~~4~~ → Measurement

for AC

$$I_m = \frac{I \times R_{sh}}{\sqrt{(R+R_{sh})^2 + \omega^2 L^2}}$$

$$\Rightarrow \frac{50 \times 0.01}{\sqrt{(0.1)^2 + (50)^2 (50)^2 \times 10^{-12}}}$$

$$\Rightarrow \frac{50 \times 0.01}{\sqrt{0.01 + 2500 \times 0.001 \times 10^{-12}}}$$

$$\Rightarrow \frac{0.5}{\sqrt{0.01 + 25 \times 0.01 \times 10^{-8}}}$$

$$\Rightarrow \frac{0.5}{\sqrt{0.01 + 0.00002025}}$$

$$\Rightarrow \frac{0.5}{0.100101199} = 4.99 \approx 5$$

Q2) The inductance of a moving iron ammeter is given by the expression

$L = (10 + 50\theta - 2\theta^2)$ mH where θ is the angular deflection in radian from zero position. Determine the angular

deflection for a current of 10A, if the deflection for a current of 5A is 30° . Also determine the screen constant.

$$\text{Soln} \quad \frac{dL}{d\theta} = \frac{2K\theta}{I^2} \Rightarrow I = SA, \theta = 30^\circ \Rightarrow \frac{1}{6}$$

$$(5 - 4 \times \frac{1}{6}) \times 10^{-6} = \frac{2 \times K \times \frac{1}{6}}{25}$$

$$K = 69.36 \times 10^{-6} \text{ Nm/rad.}$$

$$I = 10 \text{ A} \quad \theta = ? \quad \frac{dL}{d\theta} = \frac{2K\theta}{I^2} \Rightarrow (5 - 4\theta) \times 10^{-6} = \frac{2 \times 69.36 \times 10^{-6}}{10^2}$$

Q3) The inductance of a moving Iron instrument is given by $L = (0.01 + K_1 \theta)^2 \mu H$, where θ is angular deflection in radians from zero position. The instrument angular deflections corresponding to current of 2A and SA are 45° and 90° respectively, find the value of K_1 .


Errors in Moving Iron Instruments

Errors with both ac & dc

- (i) Hysteresis Error
- (ii) Temperature error
- (iii) Strong Magnetic field.

Errors with Ac only.

Frequency error

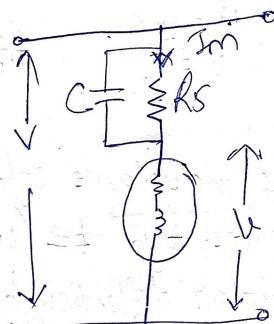

$$Z = R + j\omega L + \frac{R_S}{1 + j\omega C R_S^2}$$

$$= R + j\omega L + \frac{R_S(1 - j\omega C R_S)}{1 + \omega^2 C^2 R_S^2}$$

$$= R + j\omega L + \frac{R_S}{1 + \omega^2 C^2 R_S^2} - \frac{j\omega C R_S^2}{1 + \omega^2 C^2 R_S^2}$$

$$R + R_S = R + j\omega L + \frac{R_S}{1 + \omega^2 C^2 R_S^2} - \frac{j\omega C R_S^2}{1 + \omega^2 C^2 R_S^2}$$

$$R + R_S = R + \frac{R_S}{1 + \omega^2 C^2 R_S^2}$$

$$1 + \omega^2 C^2 R_S^2 = 1 \quad \left| \begin{array}{l} \text{if } \omega^2 C^2 R_S^2 \ll 1 \end{array} \right.$$

$$L - \frac{CR_S^2}{1 + \omega^2 C^2 R_S^2} = 0$$

$$L = \frac{CR_S^2}{1 + \omega^2 C^2 R_S^2}$$

$$L = CR_S^2$$

$$C = \frac{L}{R_S^2}$$

$$C = 0.41 \frac{L^2}{R_S^2}$$

Eddy Current

$$I_e = \omega M I$$

$$\downarrow \sqrt{R_e^2 + \omega^2 L_e^2}$$

$$I_e' = I_e \sin \theta e$$

$$= \frac{\omega M I}{\sqrt{R_e^2 + \omega^2 L_e^2}} \times \frac{\omega L_e}{\sqrt{R_e^2 + \omega^2 L_e^2}} = \frac{\omega^2 M I L_e}{R_e^2 + \omega^2 L_e^2}$$

(M)

$$E_e = \omega M I$$

$$\downarrow \\ I_e$$

↓

If $R_e \gg W_L$

$W_L \gg R_e$

$$I_e' = \omega^2 M I_c$$

$$I_e' = \frac{M I}{L_e}$$

A coil of a 300V Moving Iron Voltmeter has a resistance of 500Ω and an Inductance of 0.8H, The instrument reads correctly at 50Hz ac Supply and takes 100mA at full scale deflection, what % error in the instrument when it is connected to 200V dc Supply?

$$\underline{\text{Soln}} \quad R_m = 500\Omega$$

$$L = 0.8H$$

$$f = 50\text{Hz}$$

$$I_m = 100\text{mA} = 0.1A$$

$$X_L = 2\pi f L$$

$$= 2 \times 3.14 \times 50 \times 0.8$$

$$= 251.2 \Omega$$

$$V = 300V$$

$$\underline{\text{Soln}} \quad Z = V/I, \quad = \frac{300}{0.1} = 3000\Omega.$$

$$R = \sqrt{Z^2 - X_L^2}$$
$$= 2989.4\Omega$$

200V ac

$$I = \frac{200}{Z} = \frac{200}{3000} = 0.0667A$$

200V dc

$$I = \frac{200}{2989.4} = 0.0669A$$

0.666 → 200V

0.669 → $\frac{200 \times 0.1}{0.666} = 300V$

→ 200V

The operating coil of a 250V moving iron voltmeter has a resistance of 500Ω and Inductance of 1H. The series resistance is 2000Ω. The instrument reads correctly when a direct voltage of 250V is applied. What will it read when 250V at 50Hz is applied.

→ with what value of Capacitance must the series resistance be shunted to make the meter read correctly at 50Hz.

Soln

$$R_m = 500\Omega$$

$$R_s = 2000\Omega$$

$$L = 1H$$

~~$$f = 50\text{Hz}$$~~

$$\omega = 2\pi f$$

$$Z = \sqrt{(R+R_s)^2 + \omega^2 L^2}$$

$$= \sqrt{(2500)^2 + (100\pi)^2}$$

$$= 2519.6\Omega$$

$$R_T = R + R_s$$

$$= 2000 + 500 = 2500$$

for dc

$$I_m = \frac{250}{2500} \Rightarrow 0.1A$$

for AC

$$I_m = \frac{250}{259.6} = 0.099$$

$$0.1 \rightarrow 250V$$


$$0.099 \rightarrow \frac{250}{0.1} \times 0.099$$

$$\Rightarrow 247.5$$


$$\% \text{ error} = \frac{247.5 - 250}{250} \times 100 = (-1\%)$$

$$C = 0.41 \times \frac{1}{2000^2}$$


ELECTRODYNAMOMETER TYPE INSTRUMENTS

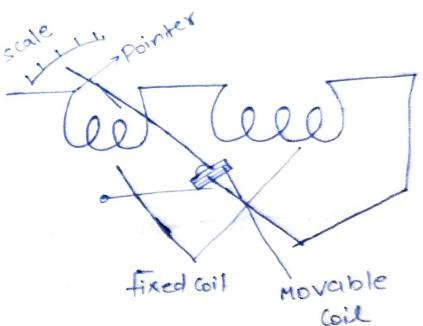


Dynamometer type Ammeter

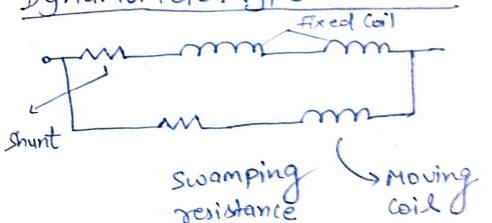

Dynamometer type Voltmeter

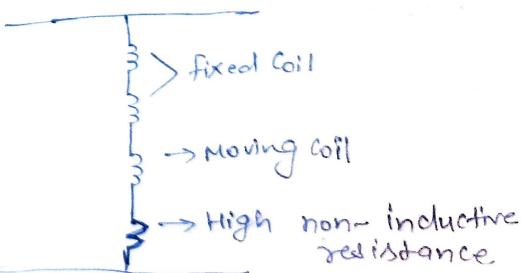

Torque equation:-

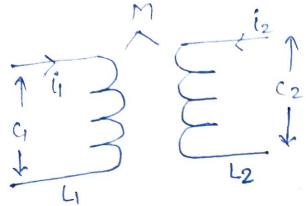

$$\text{flux linkage in Coil 1} \quad \Psi_1 = L_1 i_1 + M i_2$$

$$\text{" " " " } \quad \Psi_2 = L_2 i_2 + M i_1$$

$$e_1 = \frac{d\Psi_1}{dt}, \quad e_2 = \frac{d\Psi_2}{dt}$$

$$\therefore \text{electrical input energy} = e_1 i_1 dt + e_2 i_2 dt$$

$$= \frac{d\Psi_1}{dt} \times i_1 \times dt + \frac{d\Psi_2}{dt} \times i_2 \times dt$$

$$\Rightarrow d(L_1 i_1 + M i_2) \times i_1 + d(L_2 i_2 + M i_1) \times i_2$$

$$\Rightarrow i_1 L_1 di_1 + i_1^2 dL_1 + i_1 M di_2 + i_1 i_2 dM$$

$$+ i_2^2 dL_2 + i_2 L_2 di_2 + i_2 M di_1 + i_2 i_1 dM$$

$$\therefore \text{Stored energy} = \frac{1}{2} i_1^2 L_1 + \frac{1}{2} i_2^2 L_2 + i_1 i_2 M$$

change in stored energy:-

$$= d \left(\frac{1}{2} i_1^2 L_1 + \frac{1}{2} i_2^2 L_2 + i_1 i_2 M \right)$$

$$\Rightarrow \frac{1}{2} i_1^2 dL_1 + \frac{1}{2} L_1 di_1 + \frac{1}{2} i_2^2 dL_2 + \frac{1}{2} L_2 di_2$$

$$+ i_1 i_2 di_1 dM + i_1 M di_2 + M i_2 di_1$$

$$\Rightarrow \frac{1}{2} i_1^2 dL_1 + L_1 di_1 + \frac{1}{2} i_2^2 dL_2 + i_2 L_2 di_2 + L_1 M di_2 + i_2 M di_1$$

$$+ i_1 i_2 di_1 dM$$

Principle of conservation of energy elec. i/p energy
= change in stored energy + Mech. work done.

$$i_1 L_1 di_1 + i_1^2 dL_1 + i_1 M di_2 + i_1 i_2 di_1 dM + i_2^2 dL_2 + i_2 L_2 di_2$$

$$+ i_2 M di_1 + i_2 i_1 di_2 = \frac{1}{2} i_1^2 dL_1 + i_1 L_1 di_1 + \frac{1}{2} i_2^2 dL_2$$

$$+ i_2 L_2 di_2 + i_1 M di_2 + i_2 M di_1 + i_1 i_2 dM$$

$$+ Td.d\theta$$

$$\frac{1}{2} i_1^2 dL_1 + \frac{1}{2} i_2^2 dL_2 + i_1 i_2 dM = Td.d\theta.$$

If self inductance is constant then, $dL_1 = dL_2 = 0$

$$i_1 i_2 dM = Td.d\theta.$$

$$\boxed{Td = \frac{i_1 i_2 dM}{d\theta}}$$

For DC

$I_1 = C$ through the fixed coil

$I_2 = C$ through the moving coil.

$$T_d = I_1 I_2 \frac{dM}{d\theta}$$

$$T_c = K\theta$$

$$K\theta = I_1 I_2 \frac{dM}{d\theta}$$


$$\boxed{\theta = \frac{I_1 I_2}{K} \frac{dM}{d\theta}}$$

For AC

$$T_d = i_1 i_2 \frac{dM}{d\theta}$$

Avg. torque over whole cycle
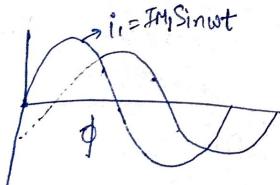
$$T_d = \frac{1}{T} \int_0^T i_1 i_2 \frac{dM}{d\theta}$$



∴ Avg. torque.

$$T_d = \frac{1}{2\pi} \int_0^{2\pi} I_{m1} \sin \omega t \times I_{m2} \sin(\omega t - \phi) \frac{dM}{d\theta} d(\omega t)$$


$$T_d = \frac{I_{m1} I_{m2} \times \cos \phi}{2} \frac{dM}{d\theta}$$

$$= \frac{I_{m1}}{\sqrt{2}} \times \frac{I_{m2}}{\sqrt{2}} \cos \phi \frac{dM}{d\theta}$$

$$\boxed{T_d = I_1 \times I_2 \cos \phi \frac{dM}{d\theta}}$$


$$K\theta = I_1 I_2 \cos \phi \frac{dM}{d\theta}$$
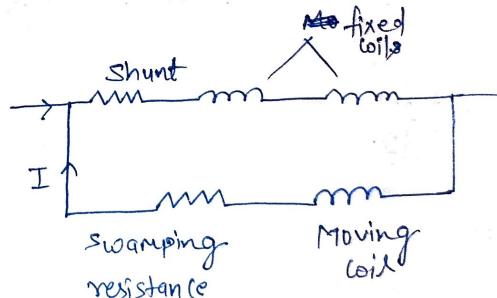
$$\boxed{\theta = \frac{I_1 I_2}{K} \cos \phi \frac{dM}{d\theta}}$$




07/09/2022

Dynamometer Ammeter

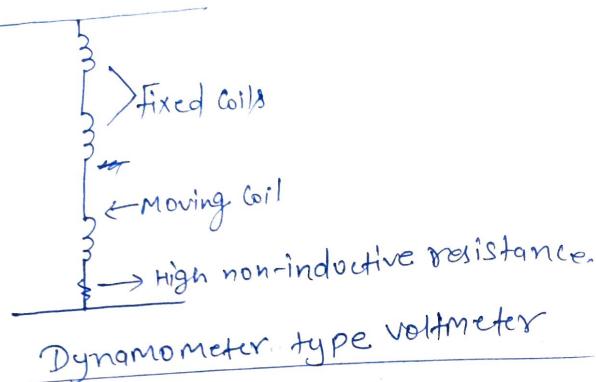

shape of scale

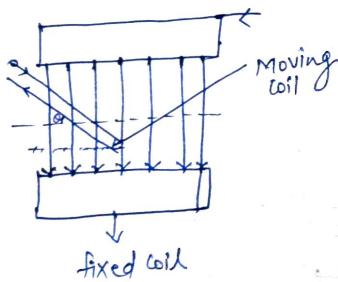

Errors

1. low torque/weight ratio
2. frequency.
3. Eddy Currents
4. External Magnetic fields.
5. Temp. change

$$\Theta = \frac{I_1 I_2}{K} \cos\phi \frac{dM}{d\theta}$$

$$I_1 = I_2 = I$$

$$\phi = 0$$

$$\therefore \Theta = \frac{I^2}{K} \frac{dM}{d\theta}$$

$$\begin{aligned} \theta &= 0^\circ \\ M &= -M_{max} \\ \text{mutual inductance for angle } \theta \Rightarrow \\ M &= -M_{max} \cos\theta \end{aligned}$$

$$\frac{dM}{d\theta} = M_{max} \sin\theta$$

$$\therefore \Theta = \frac{I_1 I_2}{K} \cos\phi M_{max} \sin\theta$$

$$\Theta = \frac{V^2}{Kz^2} \frac{dM}{d\theta}$$

$$z = \sqrt{R^2 + (2\pi f l)^2} \approx R$$

$$R_1 L_1 Z_1 ; I_1 Z_1 = I_2 Z_2$$

$$R_2 L_2 Z_2 ; \frac{I_2}{I_1} = \frac{Z_1}{Z_2} = \frac{\sqrt{R_1^2 + (2\pi f l_1)^2}}{\sqrt{R_2^2 + (2\pi f l_2)^2}}$$

$$\therefore \frac{I_1}{I_2} = R_1 \frac{\sqrt{1 + (2\pi f)^2 (\frac{L_1}{R_1})^2}}{R_2 \sqrt{1 + (2\pi f)^2 (\frac{L_2}{R_2})^2}}$$

for AC

$$\frac{I_2}{I_1} = \frac{R_1}{R_2}$$

for DC

$$\frac{I_1}{I_2} = \frac{R_2}{R_1}$$

Q The inductance of a 25Amp electrodynamic ammeter changes uniformly at the rate of 0.0035 H/degree . The spring constant is $18 \times 10^{-6} \text{ NM/degree}$. Determine the angular deflection full scale.

$$\underline{\text{Soln}} \quad \theta = \frac{I_1 I_2}{K} \cos \phi \frac{dM}{d\theta}$$

$$= \frac{I^2}{K} \frac{dM}{d\theta} = \frac{(25)^2}{10^{-6}} (35 \times 10^{-10})$$

$$\Rightarrow 625 \times 35 \times 10^{-4}$$

$$\Rightarrow 21875 \times 10^{-4}$$

$$\Rightarrow 2.1875 \text{ rad}$$

$$I = \frac{2.1875 \times 180}{\pi} = 125.33 \text{ degree}$$

$$\begin{array}{l} \text{Q81} \\ \text{II} \times \text{Sb} = 52 \\ \text{Q81} = 1 \\ \text{Q81} \leftarrow 1 \end{array}$$

The angle of full scale being 95° . If a P.D of $100V$ is applied across the voltage circuit and a current of $3A$ at a power factor of 0.75 is passed through the Current Coil, what will be the deflection if the Spring constant is $4.63 \times 10^{-6} \text{ NM/rad}$.

Soln

$$\theta = \frac{I_1 I_2}{K} \cos \phi \frac{dM}{d\theta}$$

$$= \frac{1}{82} \times 3 \times \frac{75}{100} \times 210 \times 10^{-6}$$

$$\frac{4.63 \times 10^{-6} \times \frac{\pi}{180}}{1.75 + 23}$$

$$\Rightarrow \frac{3 \times 210 \times \frac{1}{82} \times \frac{3}{4} \times 180 \times 10^{-6}}{4.63 \times 10^{-6} \times \pi}$$

$$I = \frac{V}{P} = \frac{100}{8200}$$

$$\Rightarrow \frac{1}{82}$$

$$\frac{dM}{d\theta} = \frac{175 + 23}{95 + 65}$$

$$\Rightarrow \frac{248}{99}$$

$$\frac{dm}{d\theta} = \frac{35}{2.61}$$

$$\frac{dM}{d\theta} = \frac{18000}{990} = \frac{1800}{99}$$



$$\Rightarrow \frac{3 \times 210 \times 3 \times 180}{4.63 \times \pi \times 82 \times 4} = 71.3$$

g.f. \checkmark



Q In a particular instrument the total Voltage coil is 8200Ω and Mutual Inductance and mutual inductance changes uniformly from -1234H at 0° of deflection to $+185\text{H}$ at full scale.

Measurement of Power

11/10/22

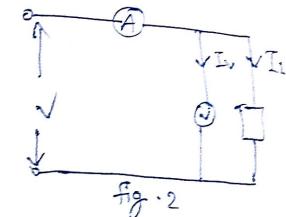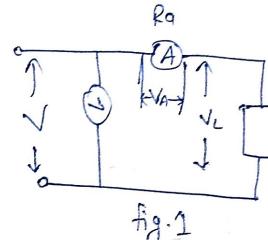

Electrodynamometer Wattmeter

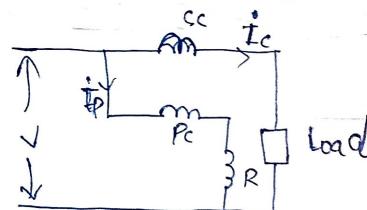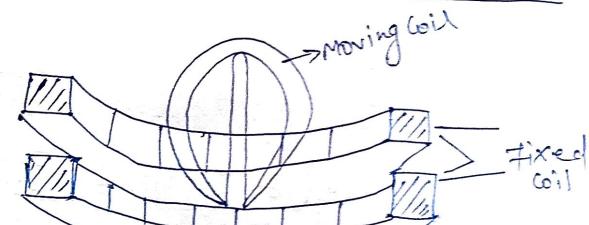

$$\text{For fig. 1} \Rightarrow P = V \times I \quad \because V = V_a + V_L$$

$$V_a = IR_a$$

$$V_L = V - V_a$$

$$\text{Power consumed by load} = IV_L$$

$$= I(V - V_a)$$

\Rightarrow Power indicated by instrument - Power lost in ammeter = $VI - V_a I$

For fig. 2 :-

Power indicated by inst. - Power consumed by load + power lost in voltmeter

$$IV = \frac{V}{R_a}$$

$$I = I_v + I_L$$

$$I_L = I - I_v$$

\therefore Power consumed by load = VI_L

$$= V(I - I_v)$$

$$= VI - \frac{V^2}{R}$$

for AC circuit

$$P = VI$$

$$V = V_m \sin \omega t$$

$$i = I_m \sin(\omega t - \phi) \quad | \quad \theta = \omega t$$

$$\therefore P = V_m \sin \omega t I_m \sin(\omega t - \phi)$$

$$= V_m I_m \sin \theta \sin(\theta - \phi)$$

$$= \frac{V_m I_m}{2} [\cos \phi - \cos(2\theta - \phi)]$$

\therefore Avg. Power over whole cycle,

$$P = \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m I_m}{2} [\cos \phi - \cos(2\theta - \phi)] d\theta$$

$$= \frac{V_m I_m}{2} \cos \phi$$

$$= \frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}} \times \cos \phi$$

$$P = VI \cos \phi$$

Torque equation -

$$T = \vec{r} \vec{l}_2 \frac{dM}{dt}$$

$$\text{and } i_c = \sqrt{2} I (\sin(\omega t + \phi)) \\ = \sqrt{2} I \sin(\omega t + \phi)$$

$$\therefore V = V_m \sin \omega t = \sqrt{2} V \sin \omega t$$

$$i_p = \frac{V}{R_p}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$i_p = \frac{V_m}{R_p} = \frac{\sqrt{2} V \sin \omega t}{R_p}$$

$$T_i = \frac{\sqrt{2}V \sin \omega t}{R_p} \times \sqrt{2} I \sin(\omega t - \phi) \frac{dM}{d\theta}$$

$$= \sqrt{2} I_p \sin \omega t \times \sqrt{2} I \sin(\omega t - \phi) \frac{dM}{d\theta}$$

$$= 2 I_p I \sin \omega t \sin(\omega t - \phi) \frac{dM}{d\theta}$$

$$= I_p I [\cos \phi - (\cos 2\omega t - \phi)] \frac{dM}{d\theta}$$

∴ Ang torque over whole cycle:

$$T_d = \frac{1}{T} \int_0^T I_p I [\cos \phi - \cos(2\omega t - \phi)] \frac{dM}{d\theta} dt$$

$$= I_p I \cos \phi \frac{dM}{d\theta}$$

$$T_d = \frac{V}{R_p} I \cos \phi \frac{dM}{d\theta}$$

$$T_c = K \theta$$

At balance

$$K \theta = \frac{V}{R_p} I \cos \phi \frac{dM}{d\theta}$$

$$\theta = \frac{V}{R_p K} I \cos \phi \frac{dM}{d\theta}$$

$$\frac{1}{R_p K} = K_1$$

$$\theta = K_1 V I \cos \phi \frac{dM}{d\theta}$$

$$\theta = K_1 V P \frac{dM}{d\theta}$$

$$\therefore \boxed{\theta \propto P}$$

12/10/2022

Errors Caused because of Correction -

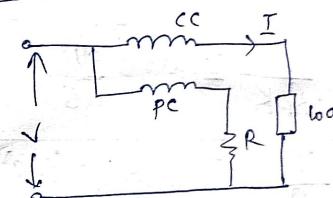


fig-a

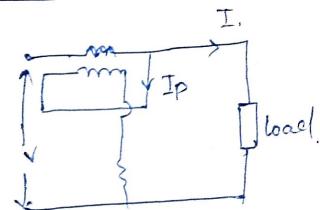


Fig-b

Wattmeter error


Pressure coil inductance



$$R_p = \gamma_p + R$$

$$Z_p = \sqrt{(R_p + R)^2 + \omega^2 L^2}$$
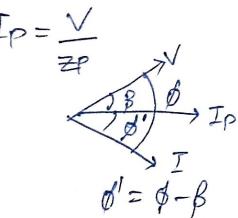
$$\frac{Z_p}{R_p} = \frac{wL}{R_p} \quad R_p = Z_p \frac{\cos \beta}{\sin \beta} \quad R_p = Z_p \frac{\cos \beta}{\sin \beta}$$



$$\theta' = \phi - \beta$$

∴ Actual wattmeter reading

$$= \frac{I_p I}{K} \cos \phi \frac{dM}{d\theta}$$

$$= \frac{I_p I}{K} \cos(\phi - \beta) \frac{dM}{d\theta}$$

$$= \frac{V}{Z_p K} I \cos(\phi - \beta) \frac{dM}{d\theta}$$

$$= \frac{V}{R_p K} I \cos(\phi - \beta) \frac{dM}{d\theta}$$

$$\Rightarrow \frac{VI}{R_p K} \cos \beta (\cos(\phi - \beta)) \frac{dM}{d\theta}$$

$$Z_p \approx Z_p \beta = 0$$

∴ True Power

$$= \frac{I_p I}{K} \cos \phi \frac{dM}{d\theta}$$


$$= \frac{V}{R_p K} I \cos \phi \frac{dM}{d\theta}$$

$$\Rightarrow \frac{\text{True Power}}{\text{Actual wattmeter reading}} = \frac{\frac{V}{R_p K} I \cos \phi \frac{dM}{d\theta}}{\frac{V}{R_p K} I \cos \beta \cos(\phi - \beta) \frac{dM}{d\theta}}$$

$$\text{True Power} = \frac{\cos \phi}{\cos \beta \cos(\phi - \beta)} \times \text{Actual wattmeter reading}$$

↓
Correction factor.

#

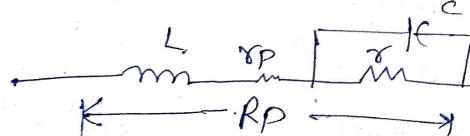

$$r_p = R_p - r$$

$$Z_p = j\omega L + (R_p - r) + \frac{r}{1+j\omega Cr}$$

$$= j\omega Lt(R_p + r) + r(1 - j\omega Cr) \quad \text{if, } \omega^2 C^2 r^2 \ll 1 + \omega^2 C^2 r^2$$

$$Z_p \approx j\omega L + R_p - r + j\omega Cr^2 \approx R_p + j\omega [L - Cr^2]$$

If we make, $L = Cr^2$

$$Z_p \approx R_p, \beta = 0$$

for fig. 1

Power indicated by wattmeter

= Power consumed by load + power loss in $I^2 R_c$

= Power consumed by load + $I^2 R_c$

for fig. 2



Power indicated by wattmeter

= Power consumed by load + power loss in R_p

$$\frac{V^2}{R_p}$$


Measurement of 3-Φ power

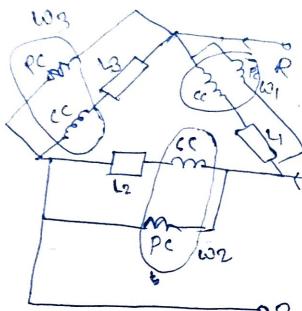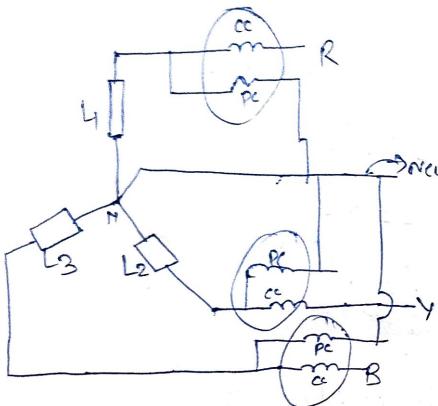1. Three Wattmeter Method.
2. Two Wattmeter Method.
3. One Wattmeter Method.



$$W_1 + W_2 + W_3 = \text{Total power of load}$$

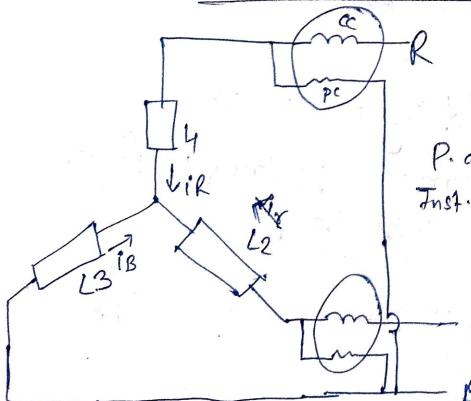Two wattmeter method for balanced/unbalanced load.



Inst. value of ct through w1 = iR

$$\text{P.d across } w_1 = e_{RB} - (e_R - e_B)$$

Inst. Power Read by w1 = $i^2 R (e_R - e_B)$

Inst. value of ct through w2 = iy

$$\text{p.d across } w_2 = e_{YB} = (e_Y - e_B)$$

Inst. Power read by w2 = $i_R i_R (e_R - e_B)$

$$W_1 + W_2 = i_R^2 R (e_R - e_B) + iy (e_Y - e_B)$$

$$= i_R^2 R - i_R e_B + iy e_Y - iy e_B$$


$$= i_R e_R + iy e_Y - e_B (iR + iy)$$

$$= \overline{P}_1 + \overline{P}_2 + \overline{P}_3$$

$$\text{Avg. Power} = \frac{1}{T} \int_0^T i_R e_R B dt + \frac{1}{T} \int_0^T iy e_Y B dt$$

13/10/2022

Two wattmeter method (Balanced load)

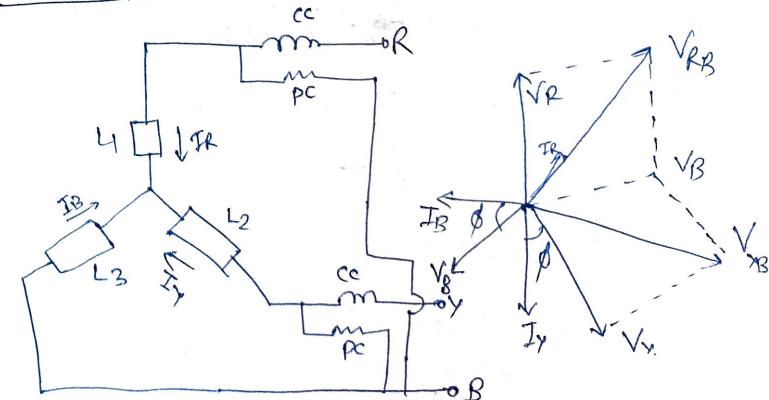

Ct through $\omega_1 = IR$

$$\text{P.d across } \omega_1 = V_{RB} = VR - VB$$

Phase diff between. \hookrightarrow Vectorially

$$IR \& V_{RB} = (30 - \phi)$$

$$\text{Reading of } \omega_1 = IR V_{RB} \cos(30 - \phi)$$

Ct through $\omega_2 = Iy$

$$\text{P.d across } \omega_2 = V_{YB}$$

$$\text{Phase difference betn } Iy \& V_{YB} = (30 + \phi)$$

$$\therefore \text{Reading of } \omega_2 = Iy V_{YB} \cos(30 + \phi)$$

$$V_{RB} = V_{YB} = VL$$

$$I_R = I_y = I_L$$

$$\omega_1 + \omega_2$$

$$= IR(V_{RB}) \cos(30 - \phi) + Iy V_{YB} \cos(30 + \phi)$$

$$= VL I_L \cos(30 - \phi) + VL I_L \cos(30 + \phi)$$

$$= VL I_L [\cos(30 - \phi) + \cos(30 + \phi)]$$

$$= \sqrt{3} VL I_L \cos \phi$$

Total power of load

$$\omega_1 + \omega_2 = \sqrt{3} VL I_L \cos \phi \quad \text{--- (i)}$$


$$\omega_1 - \omega_2 = VL I_L \sin \phi \quad \text{--- (ii)}$$

$$\tan \phi = \frac{\sqrt{3} (\omega_1 - \omega_2)}{\omega_1 + \omega_2}$$

$$\phi = \tan^{-1} \left(\frac{\sqrt{3} (\omega_1 - \omega_2)}{\omega_1 + \omega_2} \right)$$

$$\underline{\cos \phi}$$

One Wattmeter Method.

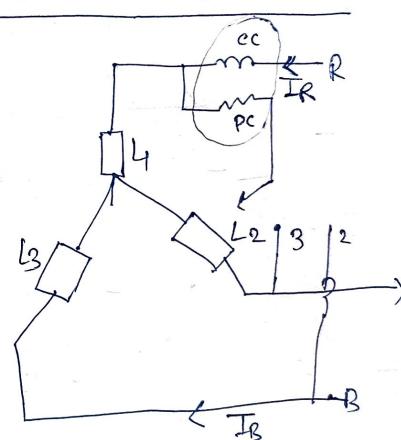

For position - 1


$$\text{Ct through } \omega_1 = IR$$

$$\text{P.d across } \omega_1 = V_{RB}$$

$$\text{Ph. diff b/w } V_{RB} \& I_R = (30 - \phi)$$

$$\Rightarrow VR = V_{RB} = VL$$
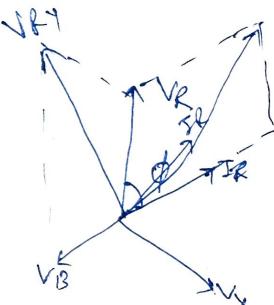
$$\begin{aligned} I_R &= I_L \\ &\Rightarrow VL I_L \cos(30 - \phi) + VL I_L (30 + \phi) \\ &= \sqrt{3} VL I_L \cos \phi \end{aligned}$$



for position - 2

$$\text{Ct through } \omega_1 = IR$$

$$\text{P.d across } \omega_1 = V_{RY}$$

$$\therefore \text{Ph. diff b/w } I_R \& V_{RY} = (30 + \phi)$$

MEASUREMENT AND MEASURING INSTRUMENTS

10/10/2022

Q.: Each phase of a 3-phase delta connected load consists of an impedance $Z = 20 \angle 60^\circ$. The line voltage is 440V at 50Hz. Compute power consumed by each phase, impedance and the total power. What will be the reading of two wattmeter connected?


Soln

$$Z = 20 \angle 60^\circ$$

$$V_{ph} = V_L = 440V$$

$$Z = 20\Omega$$

$$I_{ph} = \frac{440}{20} = 22A$$

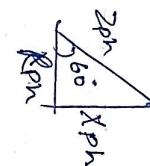

$$R_{ph} = 20 \angle 60^\circ$$


$$\therefore \text{Power/phase} = I_{ph}^2 \times R_{ph}$$

$$= 22^2 \times 10$$

$$= 4840.$$

$$\text{Total power} = 14520W.$$
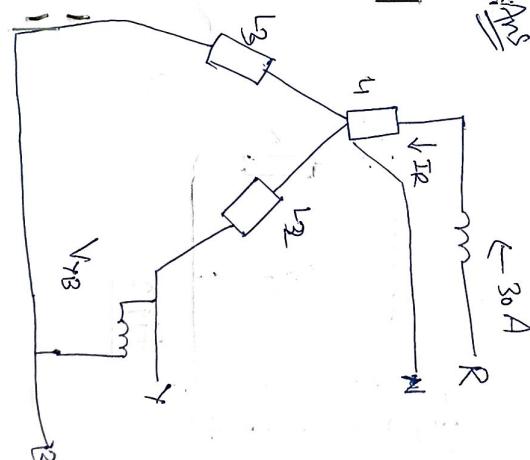
$$V_{ph} = V_L \cos(30^\circ) = \\ \omega_2 = 0$$



What does this fig. represent

Ans

$$V_P = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}}$$

$$I_P = I_L = 30A$$

$$\text{Reading} = 5.54 \times 10^3 W$$

$$\cos \phi = \frac{5540 \times 10^3}{400 \times 30}$$


$$\cos \phi = 0.999$$

$$\text{ph. diff. b/w } V_{ph} \text{ & } I_R = (90 - \phi)$$

Q.: Three identical coil each having a reading of 200 are connected in star across a 440V 50Hz line. Calculate for each method of connection the line current and the reading on each of the two wattmeter connected to measure the power.

$$\text{Reading} = V_{ph} I_R \cos(90 - \phi)$$

$$= V_{ph} I_R \sin \phi$$

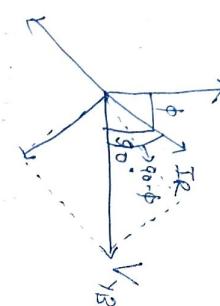

MEASUREMENT OF RESISTANCE

- i) Low resistance $< 1\Omega$
- ii) Medium resistance = 1 ohm upwards to $0.1 M\Omega$
- iii) High resistance - $0.1 M\Omega$ & upwards.

Measurement of medium resistance

- (i) Ammeter-Voltmeter Method
- (ii) Substitution Method
- (iii) Wheatstone Method
- (iv) Ohmmeter Method.

1) Ammeter-voltmeter Method :-

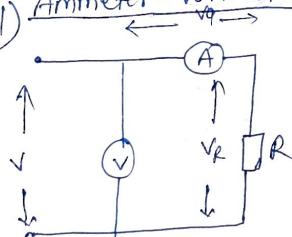


Fig. 1

$$V_a = IR_a$$

$$R_{M1} = \frac{V}{I} = \frac{V_a + V_R}{I} = \frac{IR_a + IR}{I}$$

$$R = R_{M1} - R_a \quad \therefore R_{M1} = R_a + R$$

$$= R_{M1} \left(1 - \frac{R_a}{R_{M1}} \right)^0 \Rightarrow R_{M1} - R = R_a$$

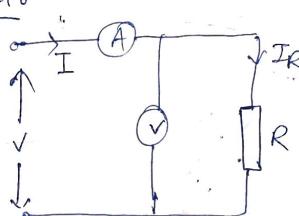


Fig. 2

$$\downarrow E_r = \frac{R_{M1} - R}{R}$$

$$= \frac{R_a}{R}$$

Fig. 2 $E_r = \frac{M-1}{T} \times 100\%$

$$R_{M2} = \frac{V}{I} = \frac{V}{IR + Ir} = \frac{V}{\frac{V}{R} + \frac{V}{R_v}} = \frac{RR_v}{R + R_v} = \frac{RR_v}{R_v(1 + \frac{R}{R_v})}$$

$$R_{M2} = \frac{R}{1 + \frac{R}{R_v}}$$

$$R_{M2} \left(1 + \frac{R}{R_v} \right) = R$$

$$R_{M2} R_v + R R_{M2} = R R_v$$

$$R R_v - R R_{M2} = R_{M2} R_v$$

$$R (R_v - R_{M2}) = R_{M2} R_v \Rightarrow R = \frac{R_{M2} R_v}{R_v - R_{M2}}$$

$$R = R_{M2} \left(\frac{1}{1 - \frac{R_{M2}}{R_v}} \right) = \frac{R_{M2} R_v}{R_v \left(1 - \frac{R_{M2}}{R_v} \right)}$$

if $R_v \ggg R_{M2}$

$$R \approx R_{M2}$$

$$R = R_{M2} \left(1 + \frac{R}{R_v} \right)$$

$$R_v \ggg R_{M2}$$

$$R \approx R_{M2}$$

$$= R_{M2} \left(1 + \frac{R_{M2}}{R_v} \right)$$

$$R_{M2} - R = -\frac{R_{M2}^2}{R_v}$$


$$\downarrow E_r = \frac{R_{M2} - R}{R} = \frac{-\frac{R_{M2}^2}{R_v}}{R} = \frac{R_{M2}^2}{R R_v} = \frac{-R^2}{R R_v} = \frac{-R}{R_v}$$

Wheatstone bridge



$R \rightarrow$ unknown resistance
 $P \rightarrow$ unknown resistance
 $S \rightarrow$ standard resistance

Wheatstone bridge

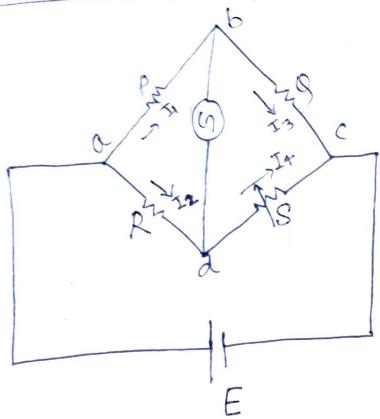

At balance-

$$\frac{I_1}{I_2} = \frac{I_3}{I_4}$$

$$I_1 = I_2$$

$$I_1 = \frac{E}{P+Q}, \quad I_2 = \frac{E}{R+S}$$

$$\frac{E}{P+Q} = \frac{E}{R+S}$$

$$\frac{P}{P+Q} = \frac{R}{R+S}$$

$$[R = \frac{P \cdot S}{P+Q}]$$

Determination of low resistance :-


1) Ammeter voltmeter method

2) Kelvin's double bridge Method

3) Potentiometer Method




Ammeter voltmeter
method.

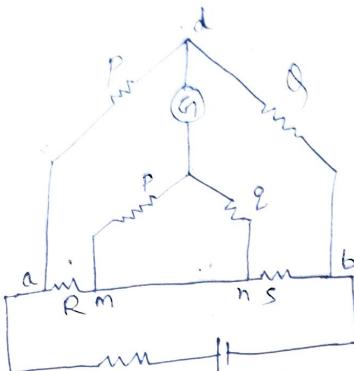

Kelvin's double bridge

$$\frac{P}{Q} = \frac{R}{S}$$

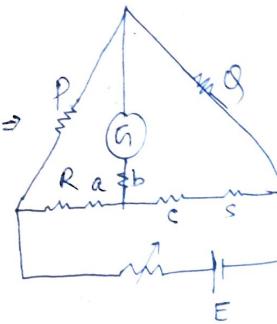

$$\frac{P}{Q} = \frac{R+a}{c+s}$$

$$b = \frac{Pq}{P+q+r}$$

$$R = \frac{P}{Q}(c+s) - a$$


$$a = \frac{Pr}{P+q+r}$$

$$= \frac{Ps + Pqr}{P+q+r} - \frac{Pr}{P+q+r}$$


$$c = \frac{qr}{P+q+r}$$

$$R = \frac{P}{Q}s + \frac{qr}{P+q+r} \left[\frac{P-b}{Q} - \frac{b}{q} \right]$$


$$[R = l \times s]$$

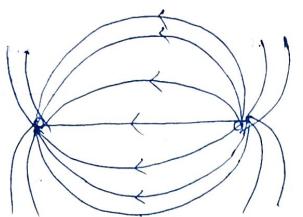

flow of ground current

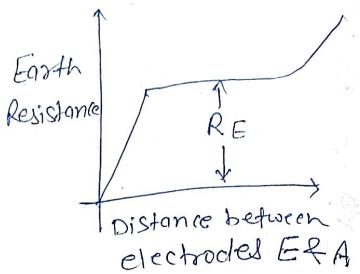

H.W High resistance (Megger)

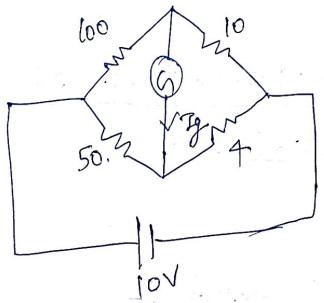

G.Ig?

$$\frac{1}{R_o} = \frac{1}{100} + \frac{1}{10} + \frac{1}{50}$$

$$R_o \Rightarrow \frac{1000}{110} + \frac{20}{5}$$

$$R_o \Rightarrow 9.09 + 3.5$$

$$R_o + g = \frac{E_0}{I_g}$$

$$10 + 12.793 = \frac{10}{I_g}$$

$$R_o = 12.793$$

$$I_g = \frac{10}{22.793} = 0.438 \text{ Amp}$$



p.d. of b w.r.t c

$$= 10 \times \frac{10}{110} = 0.909$$

p.d. of d w.r.t c

$$= 10 \times \frac{4}{59} \cancel{\approx} 0.74$$
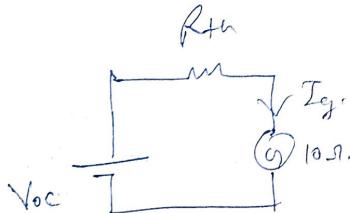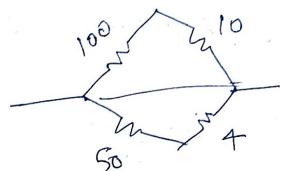
$$\begin{aligned} V_{oc} &= V_b - V_d \\ &= 0.909 - 0.74 \\ &= 0.17 \end{aligned}$$



$$R_m = (100 \parallel 10) + (50 \parallel 4) = 12.79$$

$$I_g = \frac{V_{oc}}{R_m + 10} = \frac{0.17}{12.79 + 10} = 7.45 \text{ mA}$$

Q) Three identical coils each having a resistance of 2Ω and resistance of 2Ω are connected in star and delta across a 440V, 3phase line. Calculate for each Method of connection the line current and reading of each of two wattmeter connected to measure Power. $W_1 = V_L I_L \cos(30 - \phi)$

1) Star

2) Delta

across a 440V, 3phase line. Calculate for each Method of connection the line current and reading of each of two wattmeter connected to measure Power.

$$\rightarrow W_1 = 3kW$$

$$V_P = \frac{V_L}{\sqrt{3}} = \frac{440}{\sqrt{3}}$$

$$I_P = I_L$$

$$I_P = \frac{V_P}{Z_P}$$

$$I_P = \frac{440}{\sqrt{(20)^2 + (20)^2}}$$

$$I_P = 0.984 \text{ Amp.}$$

$$= 11390.19 \text{ W}$$

$$W_2 = 3051.9941 \text{ W} \quad (14441.99)$$

Summation of
w1+w2

$$\text{Total power} = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 440 \times 0.98 \times \frac{20}{20\sqrt{2}}$$

$$= 4039.21 \text{ Watt}$$

$$W_1 = V_L I_L \cos(30 - \phi)$$

$$= 440 \times 0.98 \times 0.965 = 3816.566 \text{ W}$$

$$W_2 = V_L I_L \cos(30 + \phi) = 1022.67 \text{ W}$$

for delta

$$I_P = \frac{I_L}{\sqrt{3}}$$

$$V_P = V_L = 440$$

$$I_P = \frac{V_P}{Z_P} = \frac{V_L}{Z_P} = \frac{4}{5}$$

$$I_P = 15.55 \text{ Amp.}$$

$$I_L = \sqrt{3} I_P = 26.87 \text{ Amp.} \quad \phi = -\sqrt{3} \left(\frac{1190}{2762} \right)$$

$$W_1 = 782 \text{ W}$$

$$W_2 = 1980 \text{ W}$$

$$V_L = 416 \text{ V}$$

$$I_L = ? \quad C = ?$$

$$\tan^{-1} \left(\frac{W_1 - W_2}{W_1 + W_2} \right) = \phi$$

$$\tan \phi = -\sqrt{3} \left(\frac{1980 - 782}{1980 + 782} \right)$$

$$= -\sqrt{3} \left(\frac{1190}{2762} \right) \quad 2.53 = \frac{6838.608 \sin 36.9^\circ}{608 (30 - \phi)}$$


$$\cos \phi = 0.8$$

$$\phi = 36.9^\circ$$

$$W = \sqrt{3} V_L I_L \cos \phi$$

$$2762 = \sqrt{3} \times 416 \times I_L \times 0.8$$

$$I_L = 4.79 \text{ AMP}$$

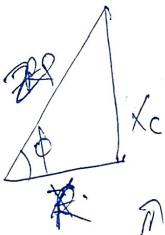

$$Z_P = \frac{V_P}{I_P}$$

$$Z_P = \frac{V_P}{I_P} = \frac{240.12}{4.79}$$

$$Z_P = 50.14 \Omega$$

$$\sin \phi = \frac{X_C}{Z_P}$$

$$0.6 = \frac{X_C}{50.14}$$

$$30.089 = X_C$$

$$\frac{1}{wC} = 30.08$$

$$= 3000 \times 31.4$$

$$C = \frac{1}{944512}$$

$$C = 1.058 \times 10^{-5}$$

~~C~~

~~27~~

Types of Cable faults

- Open circuit fault
- Short circuit fault
- Earth fault

Loop tests for location of faults in underground cable

(i) Murray loop test

(ii) Varley loop test



→ Murray loop test

$$\frac{P}{Q} = \frac{R}{X} \Rightarrow \frac{P+Q}{Q} = \frac{R+X}{X}$$


$$\Rightarrow \frac{P+Q}{Q} = \frac{R+X}{X}$$

$$X = \frac{Q}{P+Q} (R+X)$$

→ (next page)

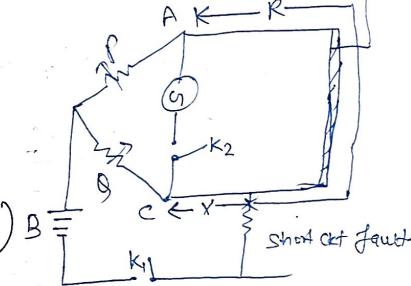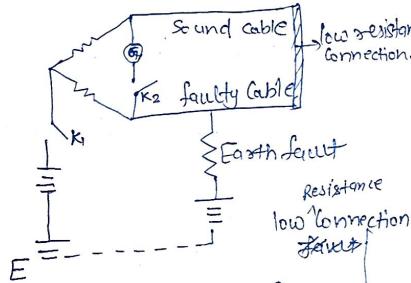

Varley loop test

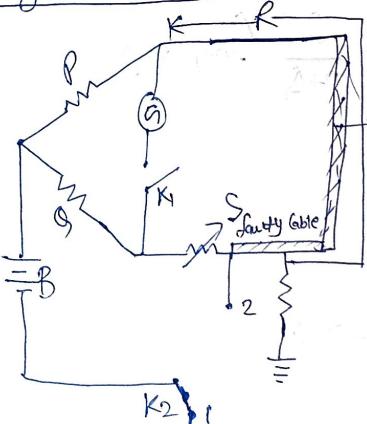

01/11/2022

Murray loop test (continued)

$$\therefore X = \frac{Q}{P+Q} (P+X)$$

γ is the resistance of each cable

$$R+X=2\gamma$$

l is the length of each cable in m.

$$\therefore \text{resistance/m length} = \gamma/l$$

$$X = \frac{Q}{P+Q} (2\gamma)$$

\therefore distance of fault from the end

$$d = \frac{X}{2\gamma l} = \frac{Q}{P+Q} \times \frac{2\gamma X l}{2\gamma}$$

$$d = \frac{Q}{P+Q} (2l)$$

$$d = \frac{Q}{P+Q} (\text{loop length})$$

Varley loop test

At position ①

At balance $S \rightarrow S_1$

$$\frac{P}{Q} = \frac{R}{X+S_1}$$

$$\frac{Q}{P+Q} = \frac{X+S_1}{P+X+S_1}$$

$$\frac{P}{Q} + 1 = \frac{R}{X+S_1} + 1$$

$$\frac{P+Q}{Q} = \frac{R+X+S_1}{X+S_1}$$

$$X = \frac{Q}{P+Q} (R+X+S_1) - S_1$$

$$X = \frac{Q(R+Q+QS_1-PS_1-S_1)}{P+Q}$$

$$X = \frac{Q(R+X)-PS_1}{P+Q}$$

At position ②

At balance $S \rightarrow S_2$

$$\frac{P}{Q} = \frac{R+X}{S_2}$$

$$\therefore R+X = \frac{P}{Q} S_2$$

$$Q(R+X) = PS_2$$

$$X = \frac{P(S_2 - S_1)}{P+Q}$$

In a test by Murray loop Method for a fault to R on a 525m length of cable having a resistance of $11.2/1000$ m, The faulty cable is looped with a sound cable of same length ~~but~~ having a resistance of $2.292/1000$ m. The resistances of the other two arm of the existing network at balance are in the ratio of 2.7 : 1. Calculate the distance of fault from testing end of cable.

Soln

% of faulty cable = $\frac{1.1}{1000}$

% of sound cable = $\frac{2.29}{1000}$

$R + X = \frac{P}{Q} S_2$

$R + X = \frac{5}{10} 16 \Rightarrow 8\Omega$

$$\left| \begin{array}{l} P = R \\ Q = S \\ X = S \cdot \left(\frac{P}{Q} \right) \end{array} \right.$$

$$R + X = \left[\frac{1.1}{1000} + \frac{2.29}{1000} \right] S_2$$

$$\Rightarrow \frac{3.39}{1000} \times 16 \Omega = 5.628 \Omega$$

$$X = \frac{5(16 - 7)}{10 + 5} \Rightarrow \frac{9}{3} = 3\Omega$$

$$d = \frac{3}{0.4} = \frac{30}{4} = \frac{15}{2} = 7.5 \text{ km}$$

$$\left| \begin{array}{l} X = \frac{(16 - 7)S}{10 + 5} \\ \Rightarrow 32 \\ d = \frac{X}{0.4} \end{array} \right.$$



$$\left| \begin{array}{l} X = \frac{Q(R + X)}{P + Q} \\ X = \frac{1}{87 + 1} \times 1.7628 \\ X = 0.476 \Omega \end{array} \right.$$

$$\left| \begin{array}{l} d = \frac{0.476}{1.1} \\ \frac{1}{1000} \\ \approx 433 \text{ m} \end{array} \right.$$

A short circuit fault is located by ~~two loop test~~ loop test. The ratios are set at $P=5\Omega$, $Q=10\Omega$ and the values of variable resistance $S=16\Omega$ for P_1 and 7Ω for P_2 .

The sound and faulty cable are identical and have a resistance of $0.45\Omega/\text{km}$. Define R as Ω/km of each cable and the distance

Anderson's bridge

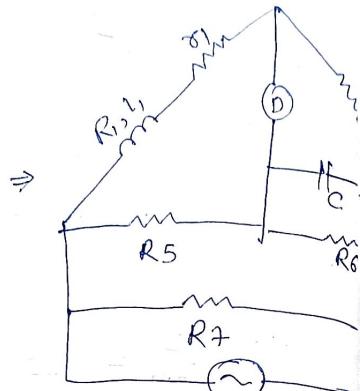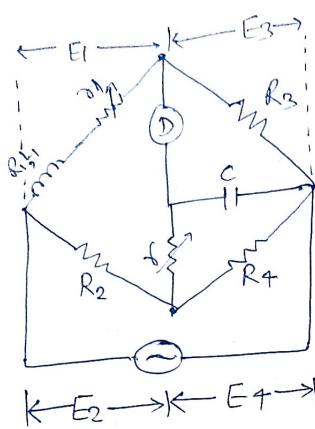


$$09/11/20 \quad j\omega LR_6 = j\omega CR_6R_5R_3$$

$$I = CR_5R_3$$

$$= C \left[\frac{R_2R_1 + \gamma R_1 + \gamma R_2}{R_1} \right] R_3$$

$$I = \frac{CR_3}{R_4} \left[\gamma(R_2 + R_4) + R_2R_4 \right]$$

phasor diagram

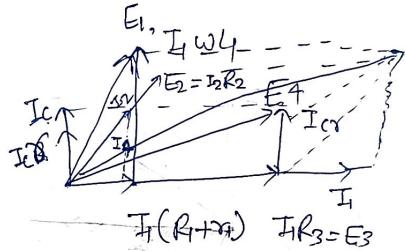

$$R_5 = R_2 + \gamma_4 + \frac{R_2\gamma}{R_4}$$

At balance.

$$R_6 = R_4 + \gamma_2 + \frac{\gamma R_4}{R_2} \left(R_1 + \gamma_1 + j\omega L_1 \right) R_6$$

$$\frac{1}{1 + j\omega CR_6}$$

$$R_7 = R_2 + R_4 + \frac{R_2R_4}{\gamma}$$

$$(R_1 + \gamma_1) R_6 = R_5 R_3$$

$$(R_1 + \gamma_1) \times \frac{(R_4 + R_2 + \gamma R_2 + \gamma R_4)}{R_2} = \frac{(R_2 R_7 + \gamma R_7)}{R_2}$$


$$\frac{R_1 \gamma_1}{R_2} = \frac{R_3}{R_4}$$

$$R_1 + \gamma_1 = R_2 R_3$$

$$R_1 = \frac{R_2 R_3}{R_4} - \gamma_1$$

Scheuring Bridge

, used to find Capacitor

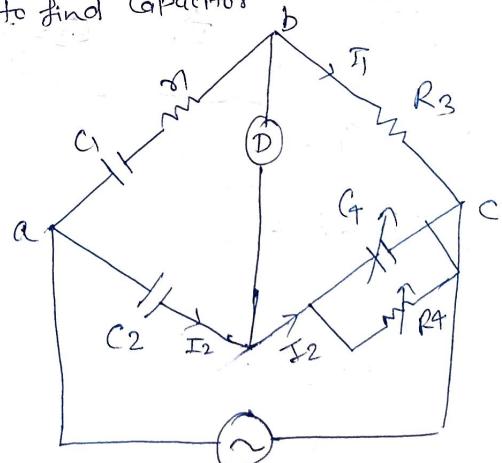

$$\boxed{Z_2 + Z_3 = Z_2 Z_3}$$

$$\left(\gamma_1 + \frac{1}{j\omega C_1} \right) \left(R_4 + j\omega L_4 \right) = \frac{R_3}{j\omega C_2}$$

$$\left(\gamma_1 + \frac{1}{j\omega C_1} \right) R_4 = \frac{R_3}{j\omega C_2} \left(1 + j\omega C_1 R_4 \right)$$

$$\left(m - \frac{1}{\omega C_1} \right) R_4 = - \frac{R_3}{\omega C_2} \left(1 + j\omega C_1 R_4 \right)$$

$$\gamma_1 = R_3 C_4 \frac{C_2}{C_1}$$


$$G_1 = \frac{R_4 C_2}{R_3}$$

$$\tan \delta = \frac{I \gamma}{\frac{I}{\omega C_1}} = \frac{\omega C_1 \gamma}{1}$$

$$\Rightarrow \omega C_1 \gamma_1$$

$$\boxed{D = \omega C_1 R_4}$$

The four arm of an AC bridge are as follows-
 The arm ab consist of a coil with inductance L_1 and resistance γ_1 in series with a non-inductive resistance (R). Arm bc and cd are each a non inductive resistance of 100Ω .
 arm ab consist of standard Variable ~~resistor~~
 inductor L_2 of resistors 92.32Ω . Balance
 is obtained when $L_2 = 47.0\text{mH}$ and $R = 1.36\Omega$.
 Find the resistance and inductance of coil in
 arm ab.

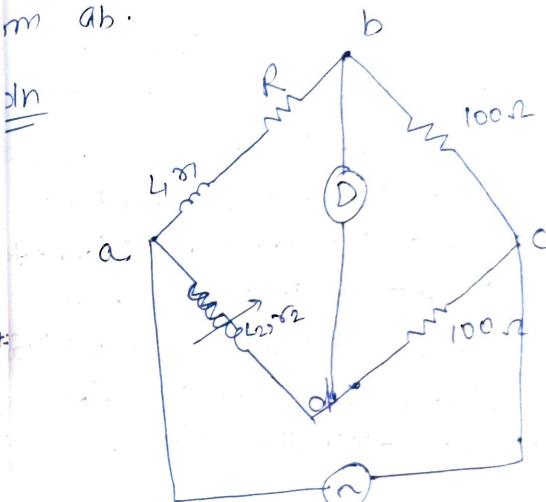

$$\boxed{Z_2 + Z_3 = Z_2 Z_3}$$

$$(R_1 + j\omega L_1 + \gamma_1) 100 = (\gamma_2 + j\omega L_2) 100$$

$$R_1 + \gamma_1 = \gamma_2$$

$$\begin{aligned} \gamma_1 &= \gamma_2 - R_1 \\ &= 37.7 - 1.36 \\ &= 36.34\Omega \end{aligned}$$

$$j\omega L_1 = j\omega L_2$$


$$L_1 = L_2$$

$$L_1 = 47.8 \text{ mH}$$

Q) The four arm of a bridge are -

Arm ab an imperfect capacitor with equivalent resistor γ_1 , arm bc a non-inductive resistance R_3 , arm cd a non-inductive resistance R_4 and arm ad an imperfect cap C_2 with an equivalent series resistance γ_2 in series with R_2 . If supply of 450 Hz is given the terminal b/w a and c and the detector is connected between b and a. At balance $R_2 = 4.8 \Omega$ and $R_3 = 2000 \Omega$, $R_4 = 2850 \Omega$, $C_2 = 0.1 \mu F$, $\gamma_2 = 0.4 \Omega$. Calculate the value of G & γ_1 and also find the dissipation factor.

Soln

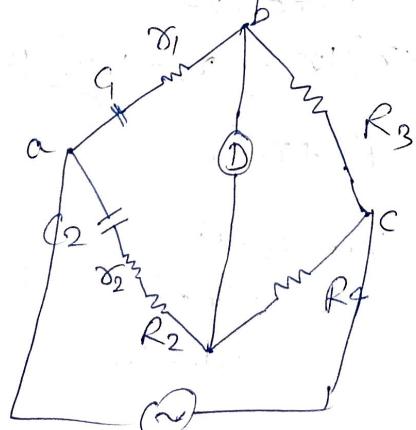

$$\left(\gamma_1 + \frac{1}{j\omega C_1} \right) R_4 = R_3 \left(R_2 + r_2 + \frac{1}{j\omega C_2} \right)$$

$$\gamma_1 R_4 + \frac{R_4}{j\omega C_1} = (R_2 + r_2) R_3 + R_3 \frac{R_4}{j\omega C_2}$$

$$\gamma_1 R_4 = (R_2 + r_2) R_3$$

$$\gamma_1 = \frac{(R_2 + r_2) R_3}{R_4} = 3.65 \Omega$$

$$D = \log \gamma_1$$

$$\frac{R_4}{j\omega C_1} = \frac{R_3}{j\omega C_2}$$

$$\frac{G}{C_4} = \frac{C_2}{R_3} \Big|_{C_1} = \frac{R_4}{R_3} C_2 = 0.7125 \text{ Hf}$$


Q) Derive the balance equation of Wien bridge and phasor diagram

A.K Sahani book, exp - 16.5, 16.7, 16.12

Accuracy, precision, sensitivity, Resolution, errors

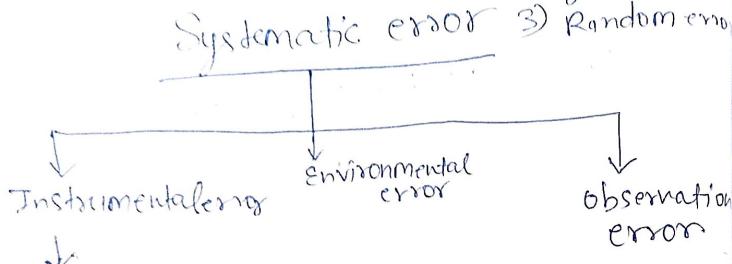- 1) Accuracy
- 2) Precision
- 3) Sensitivity
- 4) Resolution


10/11/2022
 1) static error
 2) relative static error
 3) limiting error or human error
 4) resolution
 (smallest change in value)



These errors arise due to main reasons -

- 1) Due to inherent short coming in the instrument
- 2) Due to misuse of the instrument
- 3) Due to loading effect


Observational error

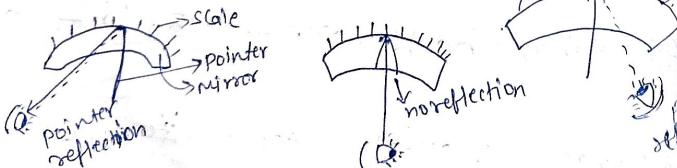


Accuracy can be expressed in the following ways -

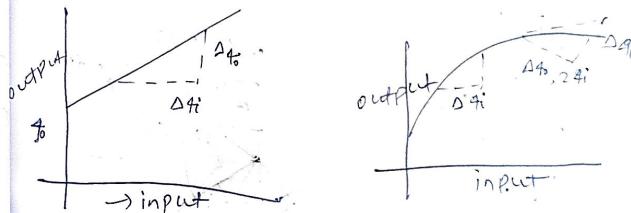- 1) point accuracy
- 2) Accuracy as percentage of scale range
- 3) Accuracy as Percentage of True value.

$$\text{sensitivity} = \frac{\text{mag. of output signal response}}{\text{mag. of input signal response}}$$




Measurement of Energy


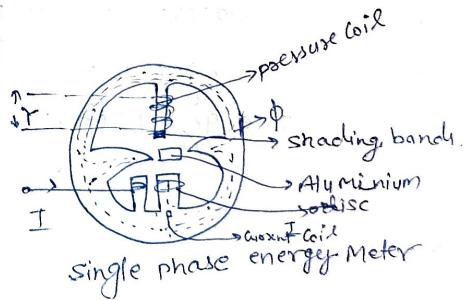


Construction

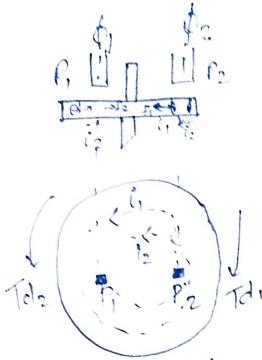- (i) Driving System
- (ii) Moving System
- (iii) Braking System
- (iv) Registering System




Working of an induction

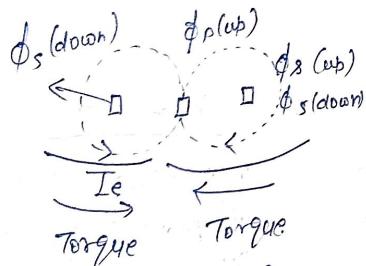
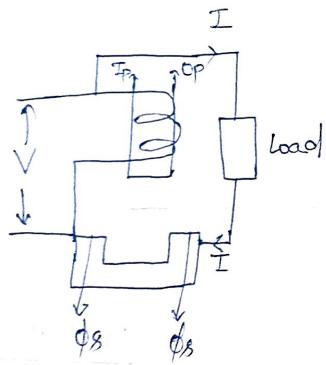


Working of single phase energy meter

Lag Adjustment device

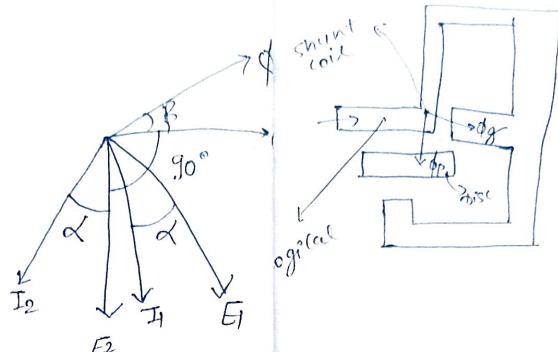

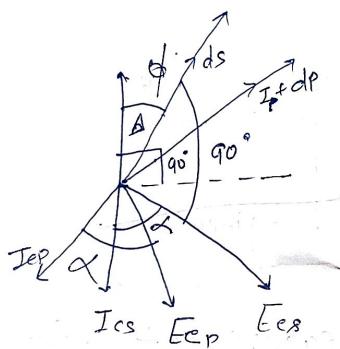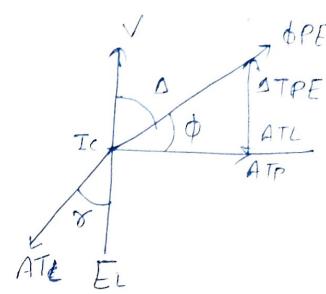phasor diagram of an induction type meter



phasor diagram of single phase energy meter

Q1) A meter constant of 230V, 10A watt-hour meter single phase is 1800 revolution/kwh. The meter is tested at half load and rated voltage and unity power factor. The meter is found to make 80 rev in 138 sec. Determine the meter error at half load.

Q2) A 230V single phase watt-hour meter has constant load of 4 AMP passing it for 6 hr At unity Power factor

If the meter disc makes 2200

during this period what is the meter constant in revolution per kWhr. Calculate the power factor of the load if the no. of revs made by the meter are 1472 when operating at 230 V, 5 Amp for 4 hrs.

$$\text{Sol-1) meter const} = \frac{\text{No. of rev}}{\text{kwhr}} \\ = 1000$$

Actual energy consumed = $\sqrt{VI} \cos \phi \times t \times 10^3$


$$= 230 \times 5 \times 1 \times \frac{138}{3600} \times$$

$$= 44.08 \times 10^{-3} \text{ kwhr}$$



$$\text{Energy recorded} = \frac{80}{1000} \Rightarrow 44.08 \times 10^{-3}$$

$$\% \text{ error} = \frac{44.4 - 44.08}{44.08} \times 100$$

Measurement of resistance

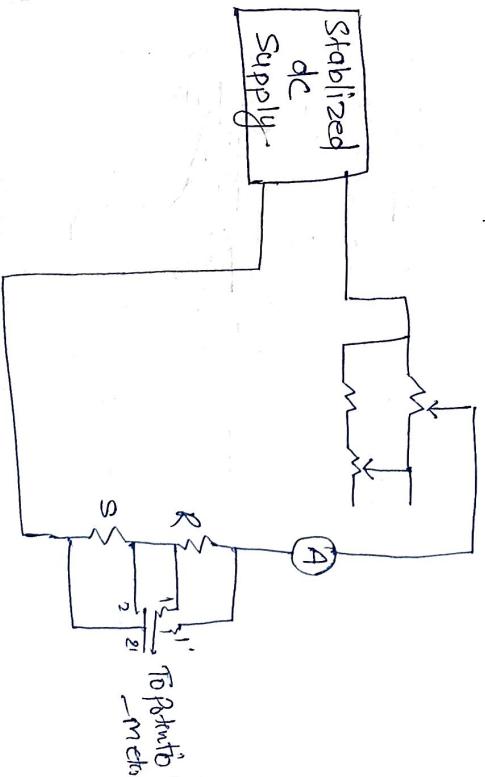

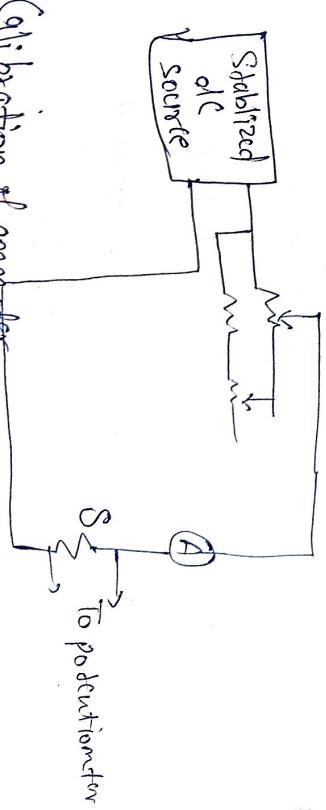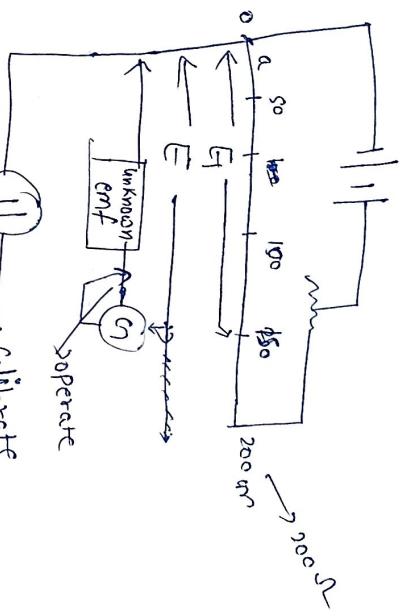Circuit diagram of basic standard potentiometer.



8004922015
1912