

B.Tech 3<sup>rd</sup> Semester End-Term Examination, 2022

SUBJECT: NETWORK ANALYSIS

CODE: UEE03B12

Full Marks: 50

Time: 2 Hrs

Answer all questions

(5x2=10)

1.

a. Find  $V_{NA}$  in Fig-1a

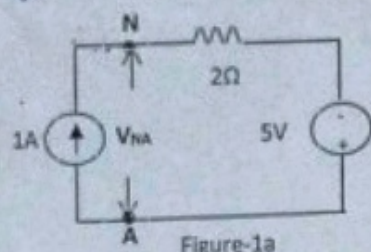


Figure-1a

b. Draw dual circuit of network shown in fig-1b

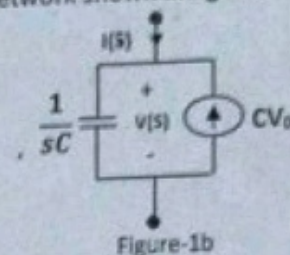


Figure-1b

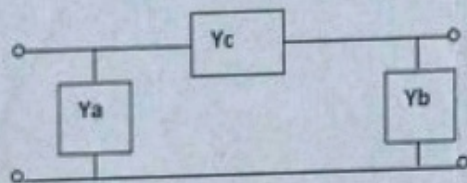


Figure-1c

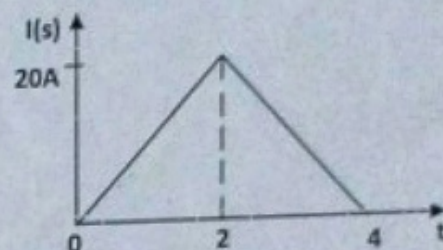


Figure-1d

c. If  $Y_{11}=8\Omega$ ,  $Y_{12}=Y_{21}=-6\Omega$  and  $Y_{22}=10\Omega$  of Fig-1c, then  $Y_a=?$ ,  $Y_b=?$  &  $Y_c=?$

d. The applied current in a 1H inductor is shown in, Fig-1d, sketch the waveform for voltage across inductor.

e. Network-A ( $N_a$ ) is 3 terminal and network-B ( $N_b$ ) is 4 terminal, connect them parallel by maintaining their own character.

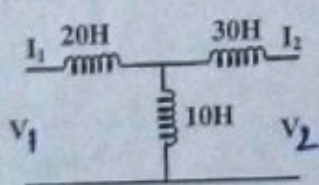


Figure-2a

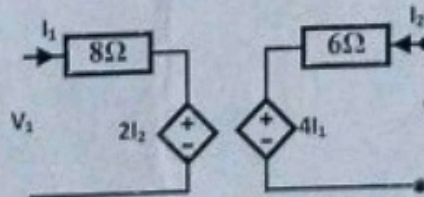


Figure-2b

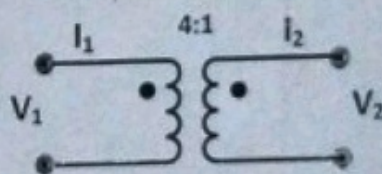


Figure-2c

(5X4=20)

2.

a. Obtain physical and mathematical  $\pi$ - network of the circuit shown in Fig-2a?

b. Draw inverse hybrid parameter equivalent circuit of network shown in Fig-2b.

c. Considering transmission parameter for the network of Fig. 1c, does it satisfied the reciprocity and symmetry condition? justify.

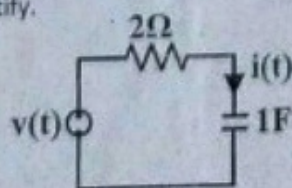


Fig. 2d

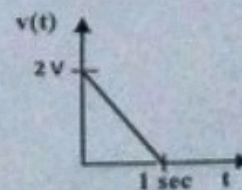


Fig. 2e



3. a. A series RC circuit of Fig. 2d is excited by a waveform shown in Fig. 2e, find current  $i(t)$ .

(10X2=20)

a.

i. Determine current  $i_L(t)$  for the network shown in Fig. 3.

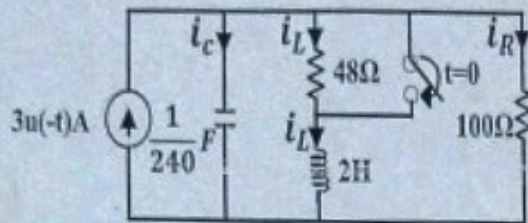


Fig. 3

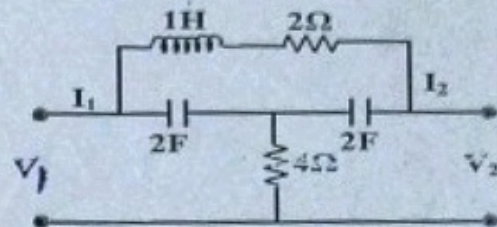


Fig. 4

ii. Determine [Y] parameter for the network shown in Fig. 4.

(5+5)

b.

Define co-efficient of coupling ( $k$ ) and indicates its value. Write the properties of 'incidence matrix'.

iii. For the coupled network shown in Fig. 5, find voltage  $V_3(t)$ , if mutual inductance  $M$  is 1H.

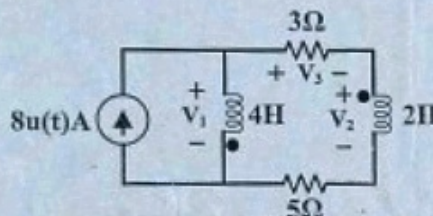


Fig. 5

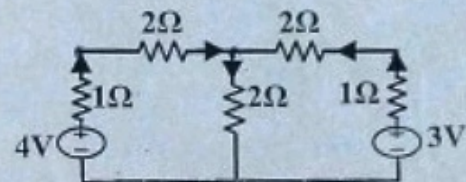


Fig. 6

iv. For the network shown in Fig. 6, write down the tie-set matrix and obtain the equilibrium equation in matrix form using KVL. Calculate loop currents and branch voltages.

v. Determine the cut-off frequency and the nominal impedance of each of the low-pass filter section shown in Fig. 7a and 7b.

(2 + 3 + 2<sup>1/2</sup> + 2<sup>1/2</sup>)

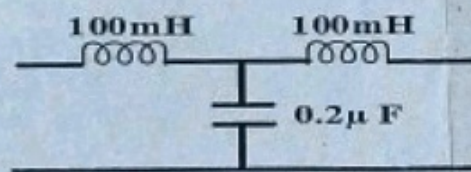


Fig. 7a

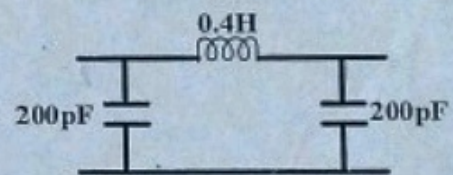


Fig. 7b