

Enrolment No. 21UEE2040

B.Tech 3rd Semester Mid-Term Examination, 2022

SUBJECT: NETWORK ANALYSIS

CODE NO: - UEE03B03

Time: 1 Hrs

Full Marks: 20

Answer all questions

1.

a. Derive the Bandwidth(BW) for series RLC circuit.

b. Determine the Thevenin equivalent impedance for the network shown in Fig.1

(2+2=4)

2.

a. For the circuit of Fig. 2, find the value of R_c for which given circuit resonates and also determines real value of admittance.b. The switch in the network of Fig. 3 has been closed since dinosaurs last walked the earth. If the switch is opened at $t=0$, find (a) $i_L(t)$ the instant after the switch change, (b) $v(t)$ at $t=0.15s$, using time domain analysis.

(4X2=8)

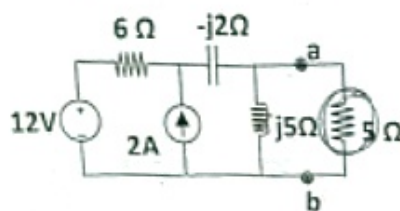


Fig. 1

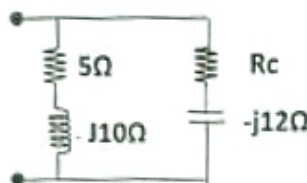


Fig. 2

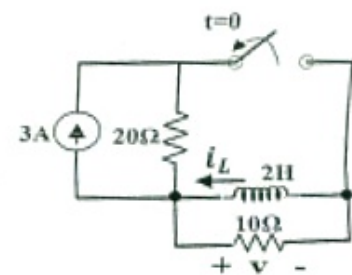


Fig. 3

3.

a. For the circuit of figure-4, find $V_c(t)$ at $t=0^-$, $t=0^+$, $t=\infty$ (infinity) and $t=0.08$ sec, using classical method.b. In the circuit of Fig. 5, find $v(t)$ for $t>0$, for $i(0^-)=1A$ and $v(0^-)=4$ volt by using laplace transformation method.

(4X2=8)

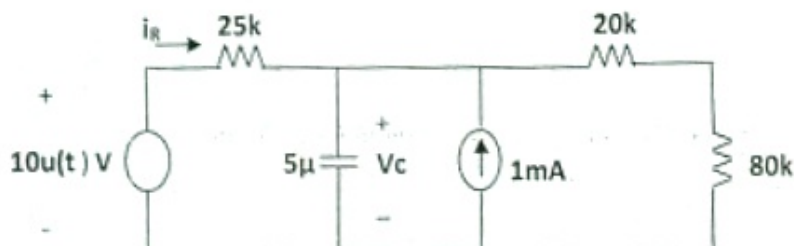


Fig. 4

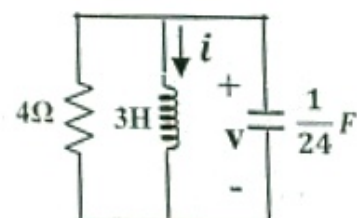


Fig. 5

Handwritten note:
 $i = 1A$
 $v = 4V$